



FinFet HSPICE Circuit Design and DRAM MATLAB Simulation

Submitted by –

Rohit Kumar Singh

Content:

Part 1 – FinFET Circuit Design

- Best Number of Fins, Fall Time, Rise Time, Fall Delay, Rise Delay
 1. 1X INV
 2. NAND
 3. NOR
- Rise Delay, Fall Delay, Rise Time, Fall Time
 1. 2X/4X INV
 2. 2X/4X NOR
 3. 2X/4X NAND
- 4 1X NOR Gate Design
 1. Rise Delay, Fall Delay, Rise Time, Fall Time
 2. Leakage Power, Switching Power
 3. Switching Energy
- 1_bit Full Adder
 1. Functional Testing
 2. Rise/Fall Delay
- Conclusion

Part 2 – DRAM Simulation in HSPICE

- 1T DRAM cell
 1. FinFet Design
 2. MOS Design
- Python Script
- DRAM.txt file, Dram_mos.txt
- MATLAB analysis file
- 3D Graph
- Python File for statistic value
- Conclusion

The Project Contains screenshots of the HSPICE file, the time datas and the waveforms along with the reported values.

INV 1X

```
1 .include './hp7nfet.pm'
2 .include './hp7pfet.pm'
3 *define parameters
4 .param vdd=0.7
5 .param vss=0
6 .param fin_height=18n
7 .param fin_width=7n
8 .param lg=11n
9 .param number_fin = 1
10 .param p_fin = 7*number_fin
11 .param n_fin = 6*number_fin
12 .param LoadCap = 1f
13 VSS Gnd 0 'vss'
14 *add transistors
15 mp1 Z Y X Y pfet L=lg NFIN=p_fin
16 mn1 Z Y 0 Y nfet L=lg NFIN=n_fin
17 *add cap
18 Cz Z Gnd 'LoadCap'
19 *add voltage source
20 VX X 0 'vdd'
21 VY Y 0 PULSE(0 0.7 0.5n 10p 10p 0.5n 1n)
22 *define the initial condition of V(Z)
23 .IC V(Z)='vdd'
24 *do transient analysis
25     *syntax: .TRAN tiner tstop START=stval
26     *tiner - time step
27     *tstop - final time
28     *stval - initial time (default 0)
29 .tran 0.01n 10n
30 *print the V(Z) to waveform file *.tr0
31 .print V(Z)
32 .print V(X)
33 .print V(Y)
34 .print i(Cz)
35 .print power(Cz)
36 *simulation options (you can modify this. Post is needed for .tran analysis)
37 .OPTION Post Brief NoMod probe measout
38 *measurement
39 .measure tran t_fall_delay TRIG V(Y) VAL = 0.35 TD = 1n
40 + RISE = 2 TARG V(Z) VAL = 0.35 FALL = 2
41 .measure tran t_rise_delay TRIG V(Y) VAL = 0.35 TD = 1n
42 + FALL = 2 TARG V(Z) VAL = 0.35 RISE = 2
43 .measure tran t_fall_time TRIG V(Z) VAL = 0.56 TD = 1n
44 + FALL = 2 TARG V(Z) VAL = 0.14 FALL = 2
45
46
47 .end
48
```

HSPICE of INV1X

```


t_fall_delay= 2.6286p  targ= 2.5076n  trig= 2.5050n
t_rise_delay= 2.7026p  targ= 2.0177n  trig= 2.0150n
t_fall_time= 3.2181p  targ= 2.5092n  trig= 2.5060n
t_rise_time= 2.9212p  targ= 2.0192n  trig= 2.0162n

```

***** job concluded

Report Details of 1X Inverter

PFIN = 7, NFIN =6

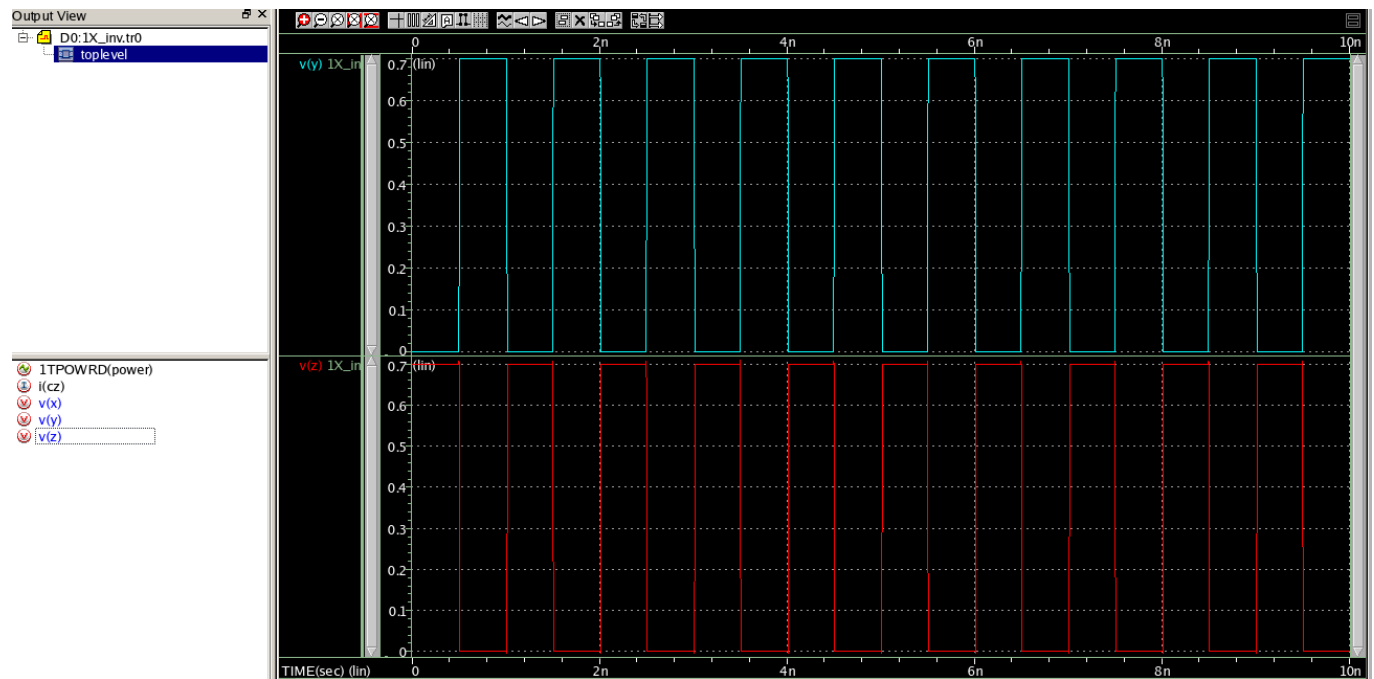

1X inverter Waveform

T_Fall_Delay = 2.6286 ps

T_Rise_Delay = 2.7026 ps

T_Fall_Time = 3.2181 ps

T_rise_Time = 2.9212 ps

NAND 1X

```

1 *****
2 *   lab3---1X_nand
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 3*number_fin
16 .param n_fin = 4*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z1 B X B pfet L=lg NFIN=p_fin
25 mn1 Z1 A Z2 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z1 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1.1u 2.2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z1)='vdd'
39
40 *do transient analysis
41     *syntax: .TRAN tiner tstop START=stval
42     *tiner - time step
43     *tstop - final time
44     *stval - initial time (default 0)

```

```

39
40 *do transient analysis
41   *syntax: .TRAN tiner tstop START=stval
42   *tiner - time step
43   *tstop - final time
44   *stval - initial time (default 0)
45 .tran 0.1u 20u
46
47 *print the V(Z) to waveform file *.tr0
48 .print V(Z1)
49 .print V(Z2)
50 .print V(X)
51 .print V(A)
52 .print V(B)
53 .print i(Cz)
54 .print power(Cz)
55
56 *simulation options (you can modify this. Post is needed for .tran analysis)
57 .OPTION Post Brief NoMod probe measout
58
59 *measurement
60 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
61 + RISE = 2 TARG V(Z1) VAL = 0.35 FALL = 2
62
63 *.measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
64 ++ RISE = 3 TARG V(Z1) VAL = 0.35 FALL = 2
65
66 *.measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
67 ++ FALL = 2 TARG V(Z1) VAL = 0.35 RISE = 2
68
69 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
70 + FALL = 3 TARG V(Z1) VAL = 0.35 RISE = 2
71
72 .measure tran t_fall_time TRIG V(Z1) VAL = 0.56 TD = 1n
73 + FALL = 2 TARG V(Z1) VAL = 0.14 FALL = 2
74
75 .measure tran t_rise_time TRIG V(Z1) VAL = 0.14 TD = 1n
76 + RISE = 2 TARG V(Z1) VAL = 0.56 RISE = 2
77
78 .end
79

```

HSPICE File of NAND1X

PFIN = 3, NFIN =4


```

d
t_fall_delay_a= 4.9134p targ= 8.8000u trig= 8.8000u
t_rise_delay_b= 4.5134p targ= 5.5000u trig= 5.5000u
t_fall_time= 4.2712p targ= 8.8000u trig= 8.8000u
t_rise_time= 4.6743p targ= 5.5000u trig= 5.5000u

```

***** job concluded

Time Details of NAND 1X

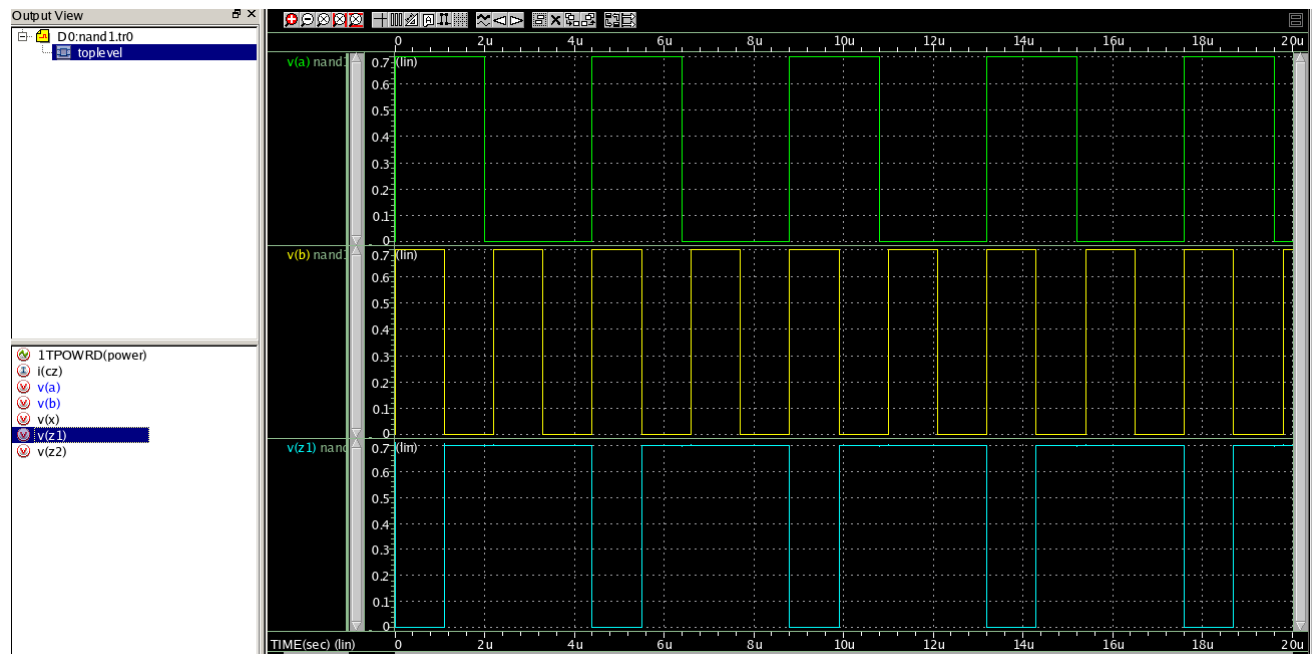

Waveform of NAND 1X

$T_{\text{Fall_Delay}} = 4.9134 \text{ ps}$

$T_{\text{Rise_Delay}} = 4.5134 \text{ ps}$

$T_{\text{Fall_Time}} = 4.2712 \text{ ps}$

$T_{\text{rise_Time}} 4.6743 \text{ ps}$

NOR 1X

```

1 *****
2 *   lab3---1X_nor
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 5*number_fin
16 .param n_fin = 3*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z2 B Z1 B pfet L=lg NFIN=p_fin
25 mn1 Z2 A 0 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z2 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2.2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1u 2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z2)='vdd'
39 .IC V(A)='vdd'
40 .IC V(B)='vdd'
41
42 *do transient analysis
43   *syntax: .TRAN tiner tstop START=stval
44   *tiner - time step

```



```

44      *tincr - time step
45      *tstop - final time
46      *stval - initial time (default 0)
47      .tran 0.1u 20u
48
49      *print the V(Z) to waveform file *.tr0
50      .print V(Z1)
51      .print V(Z2)
52      .print V(X)
53      .print V(A)
54      .print V(B)
55      .print i(Cz)
56      .print power(Cz)
57
58      *simulation options (you can modify this. Post is needed for .tran analysis)
59      .OPTION Post Brief NoMod probe measout
60      *measurement
61      .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
62      + RISE = 4 TARG V(Z2) VAL = 0.35 FALL = 6
63
64      .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
65      + RISE = 2 TARG V(Z2) VAL = 0.35 FALL = 1
66
67      .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
68      + FALL = 4 TARG V(Z2) VAL = 0.35 RISE = 5
69
70      .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
71      + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
72
73      .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
74      + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
75
76      .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
77      + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
78
79      .measure tran time1 when V(Z2)=0.14
80      .measure tran time2 when V(Z2)=0.56
81      .measure tran switching_power AVG p(Cz) from 'time1' to 'time2'
82      .measure switching_energy param = 'abs(switching_power * (time2-time1))'
83      .measure tran leakage_current AVG i(mn2) from 1u to 2u
84      .measure leakage_power param = 'abs(vdd * leakage_current)'
85      .end

```

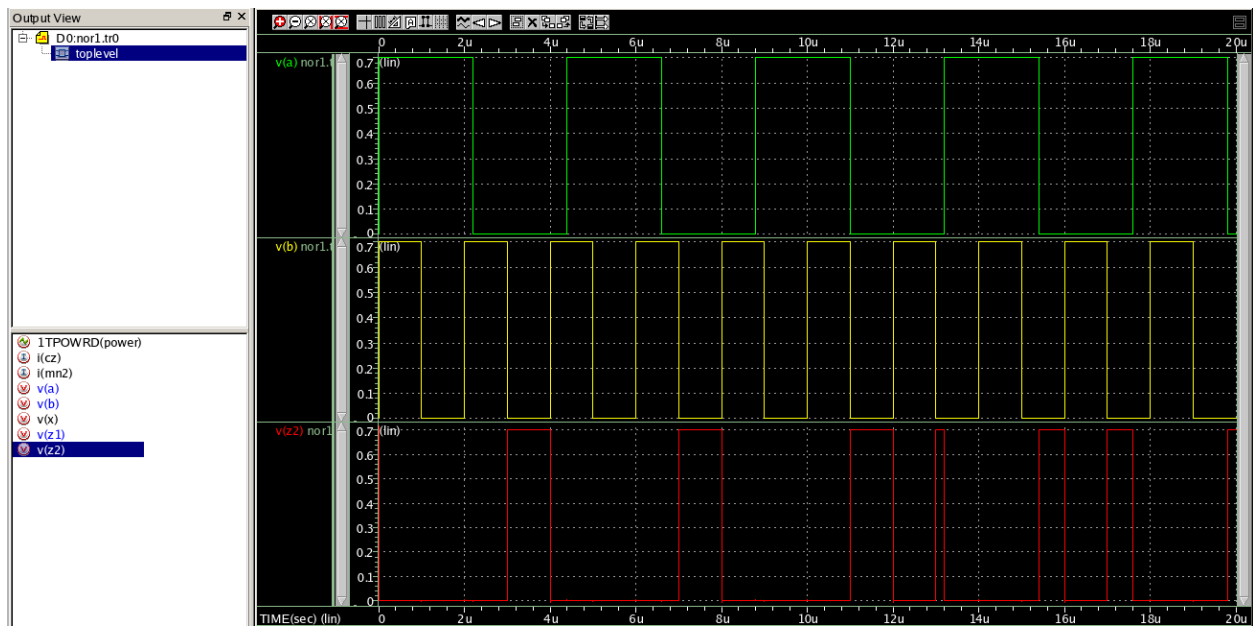

PFIN = 5, NFIN =3

```

t_fall_delay_a= 4.1131p targ= 17.6000u trig= 17.6000u
t_fall_delay_b= 3.8257p targ= 4.0000u trig= 4.0000u
t_rise_delay_a= 4.3760p targ= 15.4000u trig= 15.4000u
t_rise_delay_b= 4.2590p targ= 3.0000u trig= 3.0000u
t_fall_time= 4.3052p targ= 8.0000u trig= 8.0000u
t_rise_time= 4.8462p targ= 7.0000u trig= 7.0000u

```

##



Waveform of NOR 1X

$T_{Fall_Delay} = 4.1131 \text{ ps}$

$T_{Rise_Delay} = 4.3760 \text{ ps}$

$T_{Fall_Time} = 4.3052 \text{ ps}$

$T_{rise_Time} 4.8462 \text{ ps}$

INV 2X

```

1 *****
2 * lab3---2X_inv
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 2
15 .param p_fin = 7*number_fin
16 .param n_fin = 6*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z Y X Y pfet L=lg NFIN=p_fin
24 mn1 Z Y 0 Y nfet L=lg NFIN=n_fin
25
26 *add cap
27 Cz Z Gnd 'LoadCap'
28
29 *add voltage source
30 VX X 0 'vdd'
31
32 VY Y 0 PULSE(0 0.7 0.5n 10p 10p 0.5n 1n)
33
34 *define the initial condition of V(Z)
35 .IC V(Z)='vdd'
36
37 *do transient analysis
38 *syntax: .TRAN tiner tstop START=stval
39 *tiner - time step
40 *tstop - final time
41 *stval - initial time (default 0)
42 .tran 0.01n 10n
43
44 *print the V(Z) to waveform file *.tr0

```

```

44 *print the V(Z) to waveform file *.tr0
45 .print V(Z)
46 .print V(X)
47 .print V(Y)
48 .print i(Cz)
49 .print power(Cz)
50
51 *simulation options (you can modify this. Post is needed for .tran analysis)
52 .OPTION Post Brief NoMod probe measout
53
54 *measurement
55 .measure tran t_fall_delay TRIG V(Y) VAL = 0.35 TD = 1n
56 + RISE = 2 TARG V(Z) VAL = 0.35 FALL = 2
57
58 .measure tran t_rise_delay TRIG V(Y) VAL = 0.35 TD = 1n
59 + FALL = 2 TARG V(Z) VAL = 0.35 RISE = 2
60
61 .measure tran t_fall_time TRIG V(Z) VAL = 0.56 TD = 1n
62 + FALL = 2 TARG V(Z) VAL = 0.14 FALL = 2
63
64 .measure tran t_rise_time TRIG V(Z) VAL = 0.14 TD = 1n
65 + RISE = 2 TARG V(Z) VAL = 0.56 RISE = 2
66
67 .end
68

```

HSPICE OF INVERTER 2X

PFIN = 14, NFIN = 12


```

t_fall_delay= 1.9953p targ= 2.5070n trig= 2.5050n
t_rise_delay= 2.0015p targ= 2.0170n trig= 2.0150n
t_fall_time= 1.9609p targ= 2.5078n trig= 2.5058n
t_rise_time= 1.9445p targ= 2.0178n trig= 2.0159n

```

***** job concluded

Time Details of INV 2X

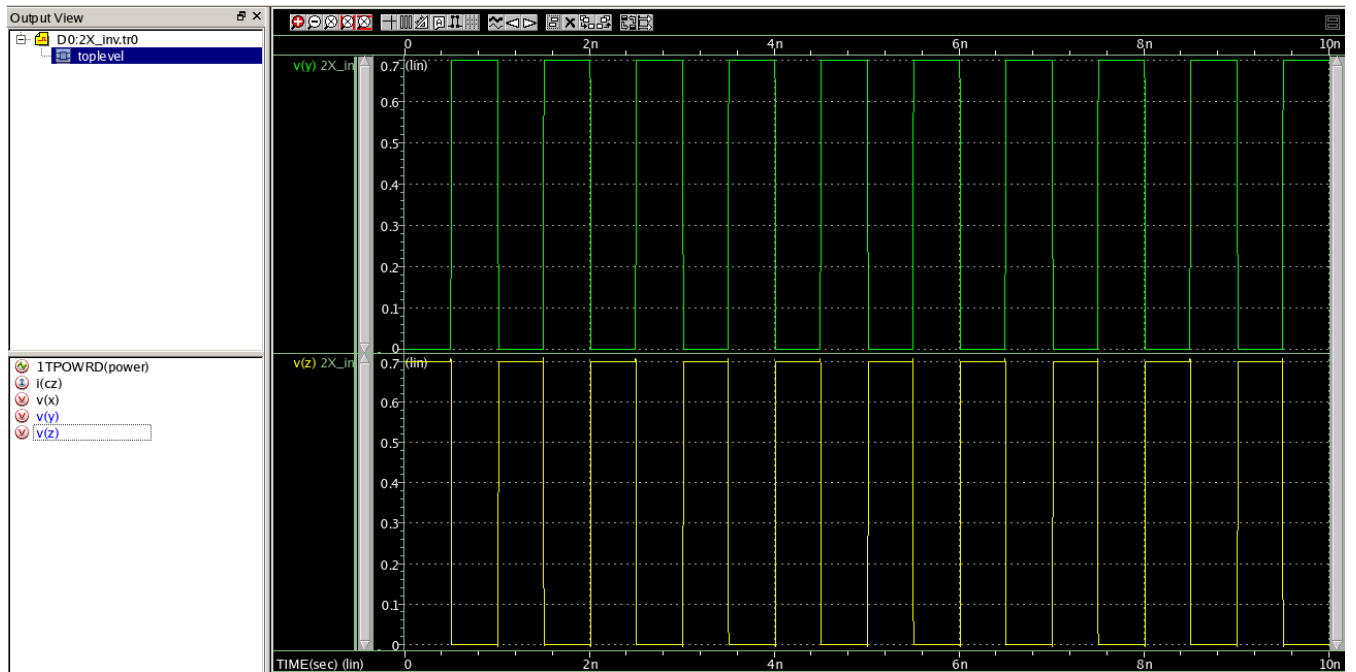

Waveform of INV 2x

$T_{\text{Fall_Delay}} = 1.9953 \text{ ps}$

$T_{\text{Rise_Delay}} = 2.0015 \text{ ps}$

$T_{\text{Fall_Time}} = 1.9609 \text{ ps}$

$T_{\text{rise_Time}} = 1.9445 \text{ ps}$

INV 4X

```

1 *****
2 * lab3--4X_inv
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 4
15 .param p_fin = 7*number_fin
16 .param n_fin = 6*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z Y X Y pfet L=lg NFIN=p_fin
24 mn1 Z Y 0 Y nfet L=lg NFIN=n_fin
25
26 *add cap
27 Cz Z Gnd 'LoadCap'
28
29 *add voltage source
30 VX X 0 'vdd'
31
32 VY Y 0 PULSE(0 0.7 0.5n 10p 10p 0.5n 1n)
33
34 *define the initial condition of V(Z)
35 .IC V(Z)='vdd'
36
37 *do transient analysis
38 *syntax: .TRAN tiner tstop START=stval
39 *tiner - time step
40 *tstop - final time
41 *stval - initial time (default 0)
42 .tran 0.01n 10n
43
44 *print the V(Z) to waveform file *.tr0

```

```

44 *print the V(Z) to waveform file *.tr0
45 .print V(Z)
46 .print V(X)
47 .print V(Y)
48 .print i(Cz)
49 .print power(Cz)
50
51 *simulation options (you can modify this. Post is needed for .tran analysis)
52 .OPTION Post Brief NoMod probe measout
53
54 *measurement
55 .measure tran t_fall_delay TRIG V(Y) VAL = 0.35 TD = 1n
56 + RISE = 2 TARG V(Z) VAL = 0.35 FALL = 2
57
58 .measure tran t_rise_delay TRIG V(Y) VAL = 0.35 TD = 1n
59 + FALL = 2 TARG V(Z) VAL = 0.35 RISE = 2
60
61 .measure tran t_fall_time TRIG V(Z) VAL = 0.56 TD = 1n
62 + FALL = 2 TARG V(Z) VAL = 0.14 FALL = 2
63
64 .measure tran t_rise_time TRIG V(Z) VAL = 0.14 TD = 1n
65 + RISE = 2 TARG V(Z) VAL = 0.56 RISE = 2
66
67 .end

```

HSPICE OF INV 4X

PFIN = 28, NFIN = 24

```

t_fall_delay= 1.3910p targ= 2.5064n trig= 2.5050n
t_rise_delay= 1.4067p targ= 2.0164n trig= 2.0150n
t_fall_time= 1.6118p targ= 2.5071n trig= 2.5055n
t_rise_time= 1.6265p targ= 2.0172n trig= 2.0155n


```

```

***** job concluded
.....

```

Time Details of INV 4X

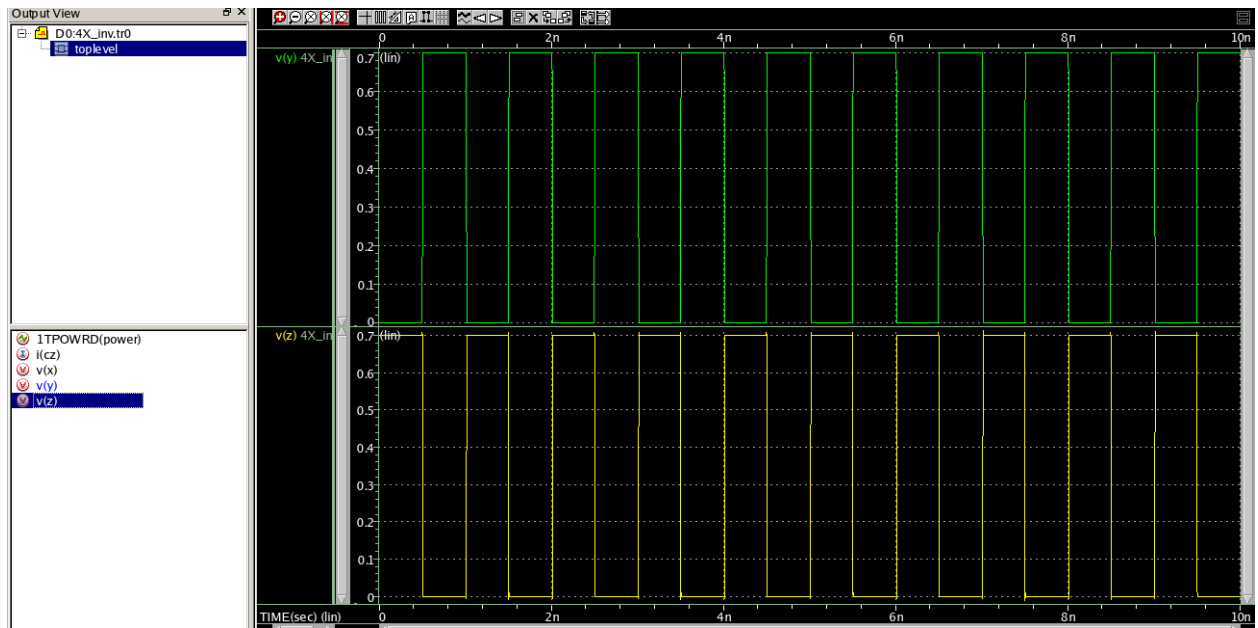

Waveform of INV 4X

$T_{\text{Fall_Delay}} = 1.3910 \text{ ps}$

$T_{\text{Rise_Delay}} = 1.4067 \text{ ps}$

$T_{\text{Fall_Time}} = 1.6118 \text{ ps}$

$T_{\text{rise_Time}} = 1.6265 \text{ ps}$

NOR 2X

```

1 *****
2 * lab3---2X_nor
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 2
15 .param p_fin = 5*number_fin
16 .param n_fin = 3*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z2 B Z1 B pfet L=lg NFIN=p_fin
25 mn1 Z2 A 0 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z2 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2.2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1u 2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z2)='vdd'
39
40 *do transient analysis
41     *syntax: .TRAN tiner tstop START=stval
42     *tiner - time step
43     *tstop - final time
44     *stval - initial time (default 0)

```

```

44      *stval - initial time (default 0)
45 .tran 0.1u 20u
46
47 *print the V(Z) to waveform file *.tr0
48 .print V(Z1)
49 .print V(Z2)
50 .print V(X)
51 .print V(A)
52 .print V(B)
53 .print i(Cz)
54 .print power(Cz)
55
56 *simulation options (you can modify this. Post is needed for .tran analysis)
57 .OPTION Post Brief NoMod probe measout
58
59 *measurement
60 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
61 + RISE = 4 TARG V(Z2) VAL = 0.35 FALL = 6
62
63 .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
64 + RISE = 2 TARG V(Z2) VAL = 0.35 FALL = 1
65
66 .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
67 + FALL = 4 TARG V(Z2) VAL = 0.35 RISE = 5
68
69 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
70 + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
71
72 .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
73 + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
74
75 .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
76 + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
77
78 .end

```

HSPICE Of NOR 2X

PFIN = 10, NFIN = 6


```

1
t_fall_delay_a= 3.3821p targ= 17.6000u trig= 17.6000u
t_fall_delay_b= 3.2519p targ= 4.0000u trig= 4.0000u
t_rise_delay_a= 3.5824p targ= 15.4000u trig= 15.4000u
t_rise_delay_b= 3.4677p targ= 3.0000u trig= 3.0000u
t_fall_time= 3.9124p targ= 8.0000u trig= 8.0000u
t_rise_time= 4.3289p targ= 7.0000u trig= 7.0000u

```

***** job concluded

Time Details of NOR2X

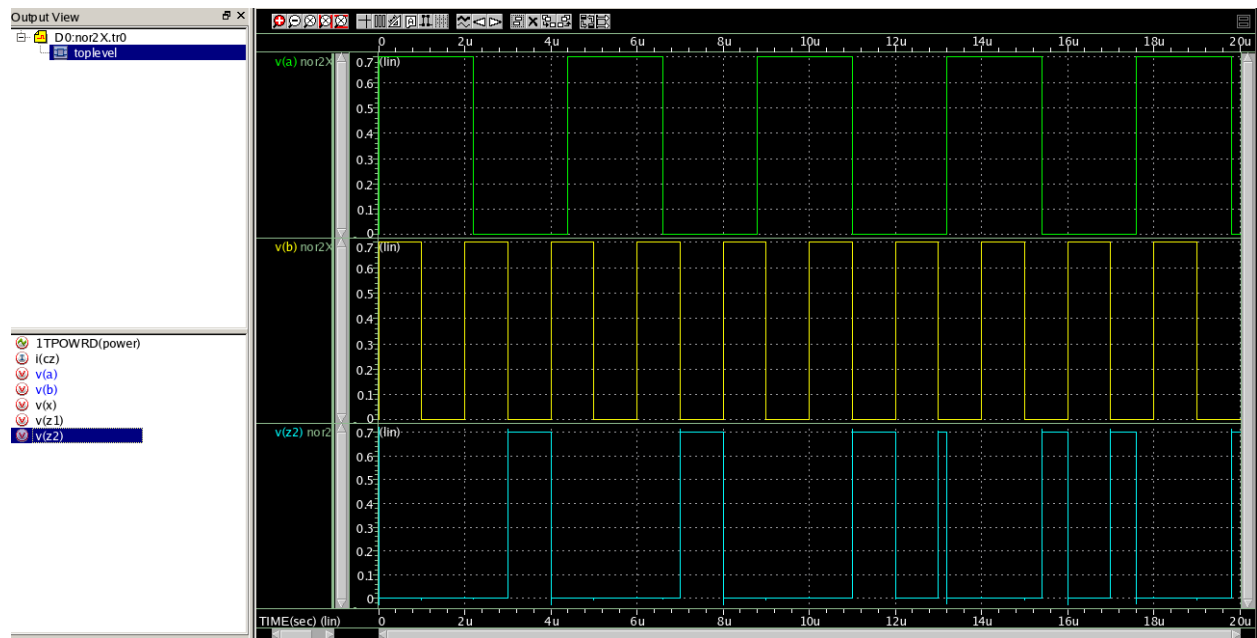

Waveform of NOR 2X

$T_{Fall_Delay} = 3.3821\text{ps}$

$T_{Rise_Delay} = 3.2519\text{ ps}$

$T_{Fall_Time} = 3.9124\text{ ps}$

$T_{rise_Time} = 4.3289\text{ ps}$

NOR 4X

```

1 *****
2 * lab3---4X_nor
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 4
15 .param p_fin = 5*number_fin
16 .param n_fin = 3*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z2 B Z1 B pfet L=lg NFIN=p_fin
25 mn1 Z2 A 0 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z2 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2.2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1u 2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z2)='vdd'
39
40 *do transient analysis
41 *syntax: .TRAN tiner tstop START=stval
42 *tiner - time step
43 *tstop - final time
44 *stval - initial time (default 0)

```

```

44      *stval - initial time (default 0)
45 .tran 0.1u 20u
46
47 *print the V(Z) to waveform file *.tr0
48 .print V(Z1)
49 .print V(Z2)
50 .print V(X)
51 .print V(A)
52 .print V(B)
53 .print i(Cz)
54 .print power(Cz)
55
56 *simulation options (you can modify this. Post is needed for .tran analysis)
57 .OPTION Post Brief NoMod probe measout
58
59 *measurement
60 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
61 + RISE = 4 TARG V(Z2) VAL = 0.35 FALL = 6
62
63 .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
64 + RISE = 2 TARG V(Z2) VAL = 0.35 FALL = 1
65
66 .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
67 + FALL = 4 TARG V(Z2) VAL = 0.35 RISE = 5
68
69 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
70 + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
71
72 .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
73 + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
74
75 .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
76 + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
77
78 .end
79

```

HSPICE OF NOR 4X

PFIN = 20, NFIN = 12


```

t_fall_delay_a= 3.1527p targ= 17.6000u trig= 17.6000u
t_fall_delay_b= 2.9954p targ= 4.0000u trig= 4.0000u
t_rise_delay_a= 3.2195p targ= 15.4000u trig= 15.4000u
t_rise_delay_b= 3.0902p targ= 3.0000u trig= 3.0000u
t_fall_time= 3.8008p targ= 8.0000u trig= 8.0000u
t_rise_time= 4.1813p targ= 7.0000u trig= 7.0000u

```

***** job concluded

Time Details of NOR 4X

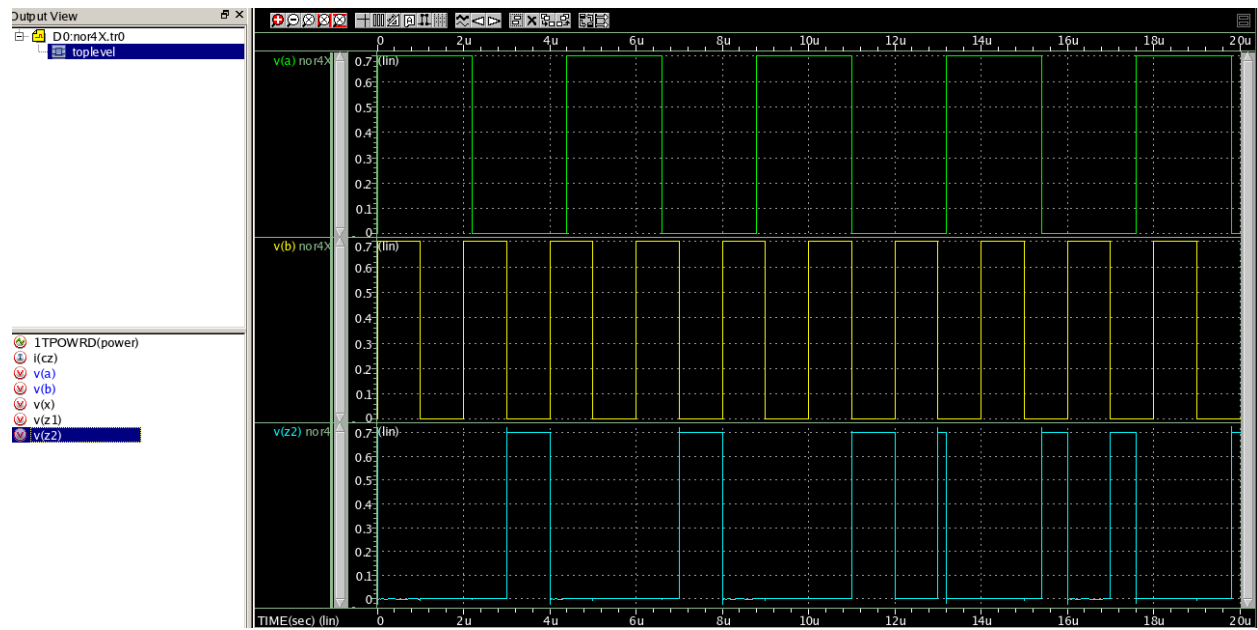

Waveform of NOR 4X

$T_{\text{Fall_Delay}} = 3.1527 \text{ ps}$

$T_{\text{Rise_Delay}} = 3.2195 \text{ ps}$

$T_{\text{Fall_Time}} = 3.8008 \text{ ps}$

$T_{\text{rise_Time}} = 4.1813 \text{ ps}$

NAND 2X

```

1 *****
2 * lab3---2X_nand
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 2
15 .param p_fin = 3*number_fin
16 .param n_fin = 4*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z1 B X B pfet L=lg NFIN=p_fin
25 mn1 Z1 A Z2 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z1 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1.1u 2.2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z1)='vdd'
39
40 *do transient analysis
41 *syntax: .TRAN tiner tstop START=stval
42 *tiner - time step
43 *tstop - final time
44 *stval - initial time (default 0)

```

```

44      *stval - initial time (default 0)
45 .tran 0.1u 20u
46
47 *print the V(Z) to waveform file *.tr0
48 .print V(Z1)
49 .print V(Z2)
50 .print V(X)
51 .print V(A)
52 .print V(B)
53 .print i(Cz)
54 .print power(Cz)
55
56 *simulation options (you can modify this. Post is needed for .tran analysis)
57 .OPTION Post Brief NoMod probe measout
58
59 *measurement
60 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
61 + RISE = 2 TARG V(Z1) VAL = 0.35 FALL = 2
62
63 *.measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
64 *+ RISE = 3 TARG V(Z1) VAL = 0.35 FALL = 2
65
66 *.measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
67 *+ FALL = 2 TARG V(Z1) VAL = 0.35 RISE = 2
68
69 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
70 + FALL = 3 TARG V(Z1) VAL = 0.35 RISE = 2
71
72 .measure tran t_fall_time TRIG V(Z1) VAL = 0.56 TD = 1n
73 + FALL = 2 TARG V(Z1) VAL = 0.14 FALL = 2
74
75 .measure tran t_rise_time TRIG V(Z1) VAL = 0.14 TD = 1n
76 + RISE = 2 TARG V(Z1) VAL = 0.56 RISE = 2
77
78 .end

```

HSPICE of NAND2X

PFIN = 6, NFIN = 8


```

t_fall_delay_a= 3.1527p targ= 17.6000u trig= 17.6000u
t_fall_delay_b= 2.9954p targ= 4.0000u trig= 4.0000u
t_rise_delay_a= 3.2195p targ= 15.4000u trig= 15.4000u
t_rise_delay_b= 3.0902p targ= 3.0000u trig= 3.0000u
t_fall_time= 3.8008p targ= 8.0000u trig= 8.0000u
t_rise_time= 4.1813p targ= 7.0000u trig= 7.0000u

```

***** job concluded

Time Details of NAND 2X

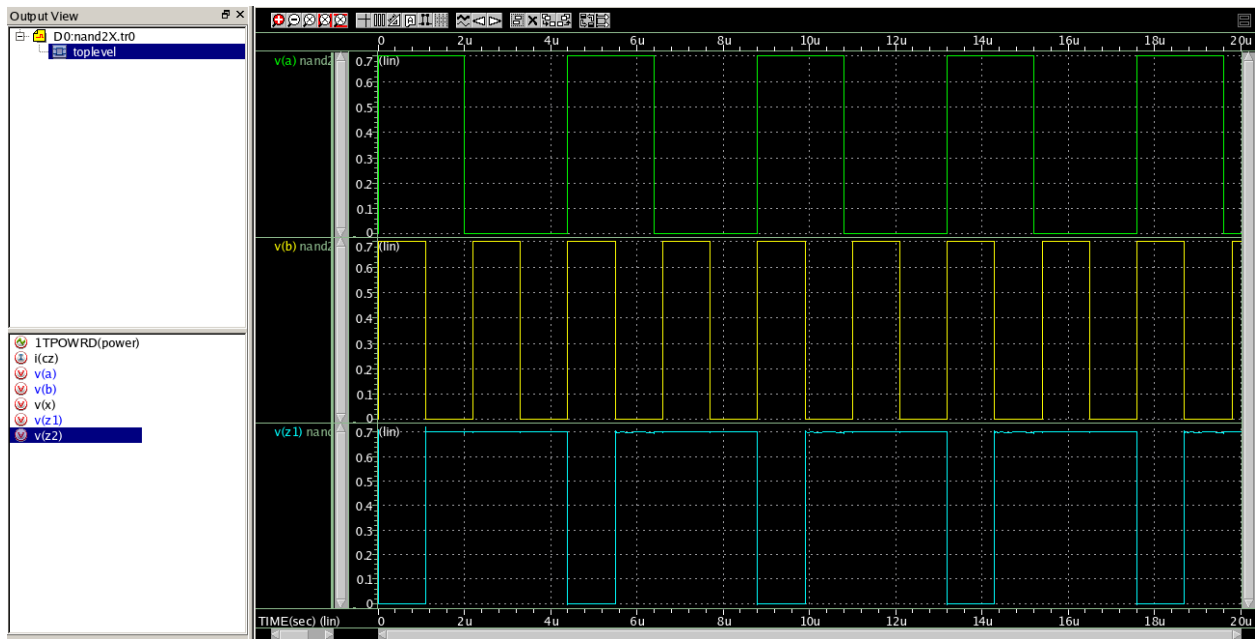

Waveform of NAND 2X

$T_{\text{Fall_Delay}} = 3.1527 \text{ ps}$

$T_{\text{Rise_Delay}} = 3.2195 \text{ ps}$

$T_{\text{Fall_Time}} = 3.8008 \text{ ps}$

$T_{\text{rise_Time}} = 4.1813 \text{ ps}$

NAND 4X

```

1 *****
2 * lab3---4X_nand
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 4
15 .param p_fin = 3*number_fin
16 .param n_fin = 4*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z1 B X B pfet L=lg NFIN=p_fin
25 mn1 Z1 A Z2 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z1 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1.1u 2.2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z1)='vdd'
39
40 *do transient analysis
41 *syntax: .TRAN tiner tstop START=stval
42 *tiner - time step
43 *tstop - final time
44 *stval - initial time (default 0)

```

```

45 .tran 0.1u 20u
46
47 *print the V(Z) to waveform file *.tr0
48 .print V(Z1)
49 .print V(Z2)
50 .print V(X)
51 .print V(A)
52 .print V(B)
53 .print i(Cz)
54 .print power(Cz)
55
56 *simulation options (you can modify this. Post is needed for .tran analysis)
57 .OPTION Post Brief NoMod probe measout
58
59 *measurement
60 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
61 + RISE = 2 TARG V(Z1) VAL = 0.35 FALL = 2
62
63 *.measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
64 ** RISE = 3 TARG V(Z1) VAL = 0.35 FALL = 2
65
66 *.measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
67 ** FALL = 2 TARG V(Z1) VAL = 0.35 RISE = 2
68
69 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
70 + FALL = 3 TARG V(Z1) VAL = 0.35 RISE = 2
71
72 .measure tran t_fall_time TRIG V(Z1) VAL = 0.56 TD = 1n
73 + FALL = 2 TARG V(Z1) VAL = 0.14 FALL = 2
74
75 .measure tran t_rise_time TRIG V(Z1) VAL = 0.14 TD = 1n
76 + RISE = 2 TARG V(Z1) VAL = 0.56 RISE = 2
77
78 .end

```

HSPICE OF NAND4X

PFIN = 12, NFIN = 16


```

t_fall_delay_a= 3.5135p targ= 8.8000u trig= 8.8000u
t_rise_delay_b= 3.2647p targ= 5.5000u trig= 5.5000u
t_fall_time= 3.4808p targ= 8.8000u trig= 8.8000u
t_rise_time= 3.8396p targ= 5.5000u trig= 5.5000u

```

***** job concluded

Time Detail of NAND 4X

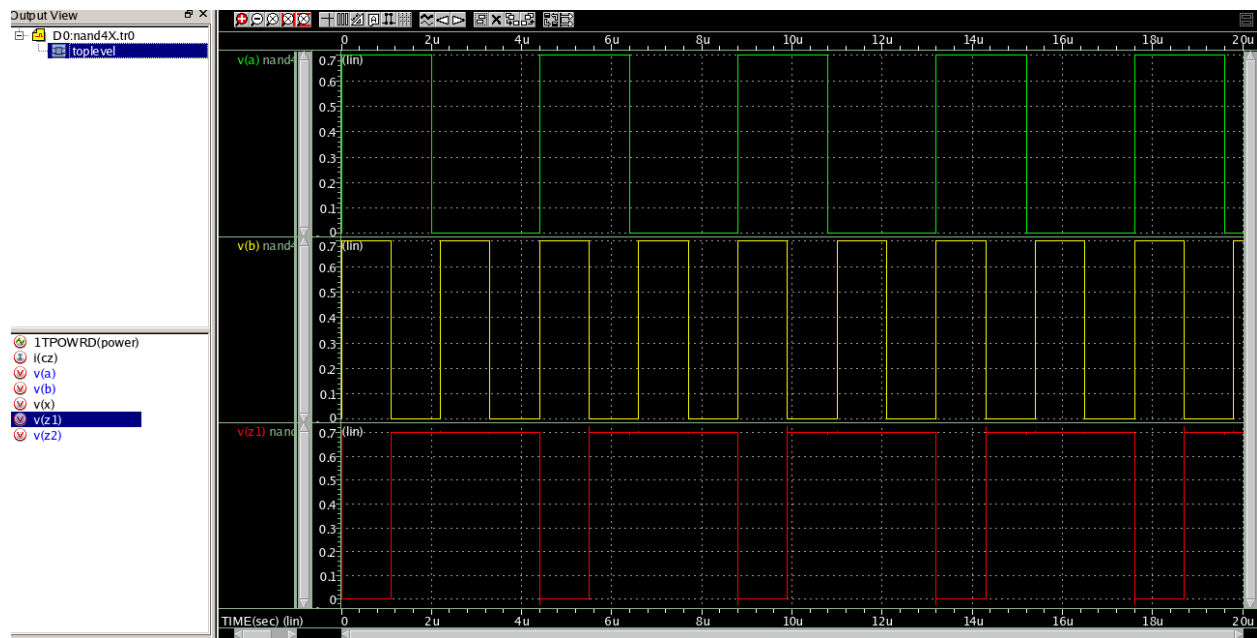

Waveform of NAND 4X

$T_{Fall_Delay} = 3.5135 \text{ ps}$

$T_{Rise_Delay} = 3.2647 \text{ ps}$

$T_{Fall_Time} = 3.4808 \text{ ps}$

$T_{rise_Time} = 3.8396 \text{ ps}$

NOR_SG

```

1 *****
2 * lab3--1X_nor
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 5*number_fin
16 .param n_fin = 3*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z2 B Z1 B pfet L=lg NFIN=p_fin
25 mn1 Z2 A 0 A nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z2 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2.2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1u 2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z2)='vdd'
39 .IC V(A)='vdd'
40 .IC V(B)='vdd'
41
42 *do transient analysis
43 *syntax: .TRAN tiner tstop START=stval
44 *tiner - time step

```

```

45      *tstop - final time
46      *stval - initial time (default 0)
47 .tran 0.1u 20u
48
49 *print the V(Z) to waveform file *.tr0
50 .print V(Z1)
51 .print V(Z2)
52 .print V(X)
53 .print V(A)
54 .print V(B)
55 .print i(Cz)
56 .print power(Cz)
57
58 *simulation options (you can modify this. Post is needed for .tran analysis)
59 .OPTION Post Brief NoMod probe measout
60 *measurement
61 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
62 + RISE = 4 TARG V(Z2) VAL = 0.35 FALL = 6
63
64 .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
65 + RISE = 2 TARG V(Z2) VAL = 0.35 FALL = 1
66
67 .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
68 + FALL = 4 TARG V(Z2) VAL = 0.35 RISE = 5
69
70 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
71 + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
72
73 .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
74 + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
75
76 .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
77 + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
78
79 .measure tran time1 when V(Z2)=0.14
80 .measure tran time2 when V(Z2)=0.56
81 .measure tran switching_power AVG p(Cz) from 'time1' to 'time2'
82 .measure switching_energy param = 'abs(switching_power * (time2-time1))'
83 .measure tran leakage_current AVG i(mn2) from 1u to 2u
84 .measure leakage_power param = 'abs(vdd * leakage_current)'
85 .end

```

HSPICE OF NOR_SG

PFIN = 5, NFIN = 3


```

t_fall_delay_a= 4.1131p targ= 17.6000u trig= 17.6000u
t_fall_delay_b= 3.8257p targ= 4.0000u trig= 4.0000u
t_rise_delay_a= 4.3760p targ= 15.4000u trig= 15.4000u
t_rise_delay_b= 4.2590p targ= 3.0000u trig= 3.0000u
t_fall_time= 4.3052p targ= 8.0000u trig= 8.0000u
t_rise_time= 4.8462p targ= 7.0000u trig= 7.0000u
time1= 8.9025p
time2= 6.1202p
switching_power= -50.4293u from= 6.1202p to= 8.9025p
switching_energy= 140.3077a
leakage_current= 7.1374p from= 1.0000u to= 2.0000u
leakage_power= 4.9962p

***** job concluded
.....

```

Time Details of NOR 1X SG

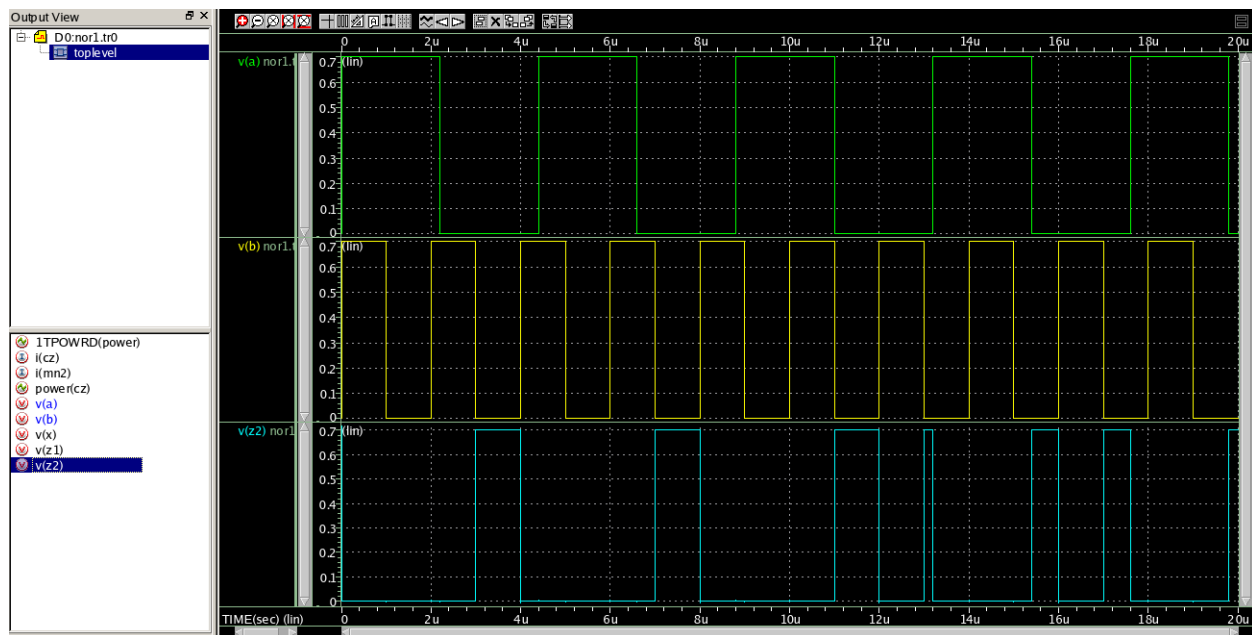

Waveform of NOR 1X SG

T_Fall_Delay = 4.1131 ps

T_Rise_Delay = 4.3760 ps

T_Fall_Time = 4.3052 ps

T_rise_Time = 4.8462 ps

Switching power = -50.4293uW

Switching energy = 140.3077aJ

Leakage current = 7.1374pAmp

Leakage power = 4.9962pW

NOR_IG

```

1 *****
2 *   lab3---1X_nor_IG
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 6*number_fin
16 .param n_fin = 2*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z2 A X B pfet L=lg NFIN=p_fin
24 mn1 Z2 A 0 A nfet L=lg NFIN=n_fin
25 mn2 Z2 B 0 B nfet L=lg NFIN=n_fin
26
27 *add cap
28 Cz Z2 Gnd 'LoadCap'
29
30 *add voltage source
31 VX X 0 'vdd'
32
33 VA A 0 PULSE(0 0.7 0 10p 10p 1.2u 2.2u)
34 VB B 0 PULSE(0 0.7 0 10p 10p 0.5u 1.1u)
35
36 *define the initial condition of V(Z)
37 .IC V(Z2)='vdd'
38
39 *do transient analysis
40 *syntax: .TRAN tiner tstop START=stval
41 *tiner - time step
42 *tstop - final time
43 *stval - initial time (default 0)
44 .tran 0.1u 20u

```



```

45
46 *print the V(Z) to waveform file *.tr0
47 .print V(Z1)
48 .print V(Z2)
49 .print V(X)
50 .print V(A)
51 .print V(B)
52 .print i(Cz)
53 .print power(Cz)
54
55 *simulation options (you can modify this. Post is needed for .tran analysis)
56 .OPTION Post Brief NoMod probe measout
57
58 *measurement
59 *.measure tran t_fall_delay_A TRIG V(A) VAL = 0.35
60 ** RISE = 4 TARG V(Z2) VAL = 0.35 FALL = 6
61
62 .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35
63 + RISE = 3 TARG V(Z2) VAL = 0.35 FALL = 2
64
65 .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35
66 + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 2
67
68 *.measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
69 ** FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
70
71 .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
72 + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
73
74 .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
75 + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
76
77 .measure tran time1 when V(Z2)=0.14
78 .measure tran time2 when V(Z2)=0.56
79 .measure tran switching_power AVG p(Cz) from 'time1' to 'time2'
80 .measure switching_energy param = 'abs(switching_power * (time2-time1))'
81
82
83 .measure tran leakage_current AVG i(mn2) from 1.1u to 2.2u
84 .measure leakage_power param = 'abs(vdd * leakage_current)'
85
86 .end

```

HSPICE File of NOR 1_IG

PFIN = 6, NFIN = 2


```

t_fall_delay_b= 3.4841p targ= 2.2000u trig= 2.2000u
t_rise_delay_a= 3.8528p targ= 3.4000u trig= 3.4000u
t_fall_time= 4.1208p targ= 4.4000u trig= 4.4000u
t_rise_time= 4.9263p targ= 3.4000u trig= 3.4000u
time1= 9.8130p
time2= 6.7983p
switching_power= -50.2411u from= 6.7983p to= 9.8130p
switching_energy= 151.4615a
leakage_current= 57.8165u from= 1.1000u to= 2.2000u
leakage_power= 40.4715u

***** job concluded
*****

```

Time Details of NOR 1X IG

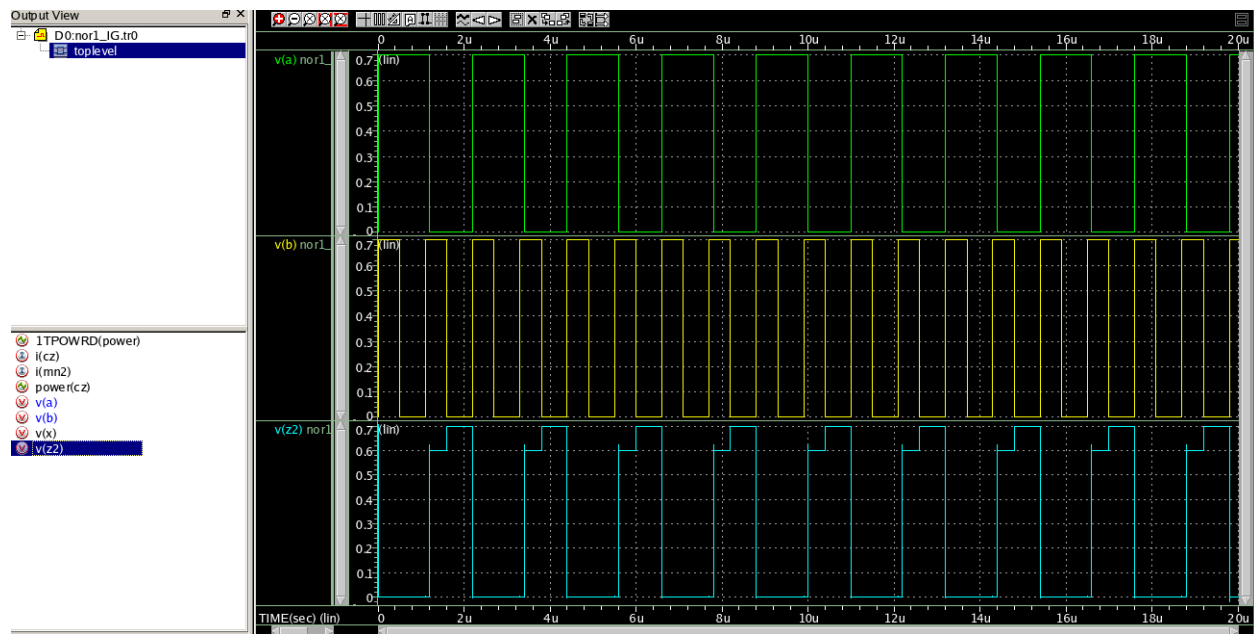

Waveform of NOR 1X IG

$T_{\text{Fall_Delay}} = 3.4841 \text{ ps}$

$T_{\text{Rise_Delay}} = 3.8528 \text{ ps}$

$T_{\text{Fall_Time}} = 4.1208 \text{ ps}$

$T_{\text{rise_Time}} = 4.9263 \text{ ps}$

Switching power = -50.241uW

Switching energy = 151.4615aJ

Leakage current = 57.8165 uAmp

Leakage power = 40.4715 uW

NOR_LP

```

1 *****
2 * lab3---1X_nor_LP
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 5*number_fin
16 .param n_fin = 3*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X X pfet L=lg NFIN=p_fin
24 mp2 Z2 B Z1 X pfet L=lg NFIN=p_fin
25 mn1 Z2 A 0 0 nfet L=lg NFIN=n_fin
26 mn2 Z2 B 0 0 nfet L=lg NFIN=n_fin
27
28 *add cap
29 Cz Z2 Gnd 'LoadCap'
30
31 *add voltage source
32 VX X 0 'vdd'
33
34 VA A 0 PULSE(0 0.7 0 10p 10p 2.2u 4.4u)
35 VB B 0 PULSE(0 0.7 0 10p 10p 1u 2u)
36
37 *define the initial condition of V(Z)
38 .IC V(Z2)='vdd'
39
40 *do transient analysis
41 *syntax: .TRAN tiner tstop START=stval
42 *tiner - time step
43 *tstop - final time
44 *stval - initial time (default 0)

```

```

45 .tran 0.1u 20u
46
47 *print the V(Z) to waveform file *.tr0
48 .print V(Z1)
49 .print V(Z2)
50 .print V(X)
51 .print V(A)
52 .print V(B)
53 .print i(Cz)
54 .print power(Cz)
55
56 *simulation options (you can modify this. Post is needed for .tran analysis)
57 .OPTION Post Brief NoMod probe measout
58
59 *measurement
60 .measure tran t_fall_delay_A TRIG V(A) VAL = 0.35 TD = 1n
61 + RISE = 4 TARG V(Z2) VAL = 0.35 FALL = 6
62
63 .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35 TD = 1n
64 + RISE = 2 TARG V(Z2) VAL = 0.35 FALL = 1
65
66 .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35 TD = 1n
67 + FALL = 4 TARG V(Z2) VAL = 0.35 RISE = 5
68
69 .measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
70 + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
71
72 .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
73 + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
74
75 .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
76 + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
77
78 .measure tran time1 when V(Z2)=0.14
79 .measure tran time2 when V(Z2)=0.56
80 .measure tran switching_power AVG p(Cz) from 'time1' to 'time2'
81 .measure switching_energy param = 'abs(switching_power * (time2-time1))'
82
83
84 .measure tran leakage_current AVG i(mn2) from 1u to 2u
85 .measure leakage_power param = 'abs(vdd * leakage_current)'
86
87 .end

```

HSPICE OF NOR1X_LP

PFIN = 5, NFIN = 3


```

y
t_fall_delay_a= 4.1131p targ= 17.6000u trig= 17.6000u
t_fall_delay_b= 3.8257p targ= 4.0000u trig= 4.0000u
t_rise_delay_a= 4.3760p targ= 15.4000u trig= 15.4000u
t_rise_delay_b= 4.2590p targ= 3.0000u trig= 3.0000u
t_fall_time= 4.3047p targ= 8.0000u trig= 8.0000u
t_rise_time= 4.8460p targ= 7.0000u trig= 7.0000u
time1= 8.9025p
time2= 6.1202p
switching_power= -50.4293u from= 6.1202p to= 8.9025p
switching_energy= 140.3077a
leakage_current= 7.1383p from= 1.0000u to= 2.0000u
leakage_power= 4.9968p

```

***** job concluded

Time Details of NOR 1X LP

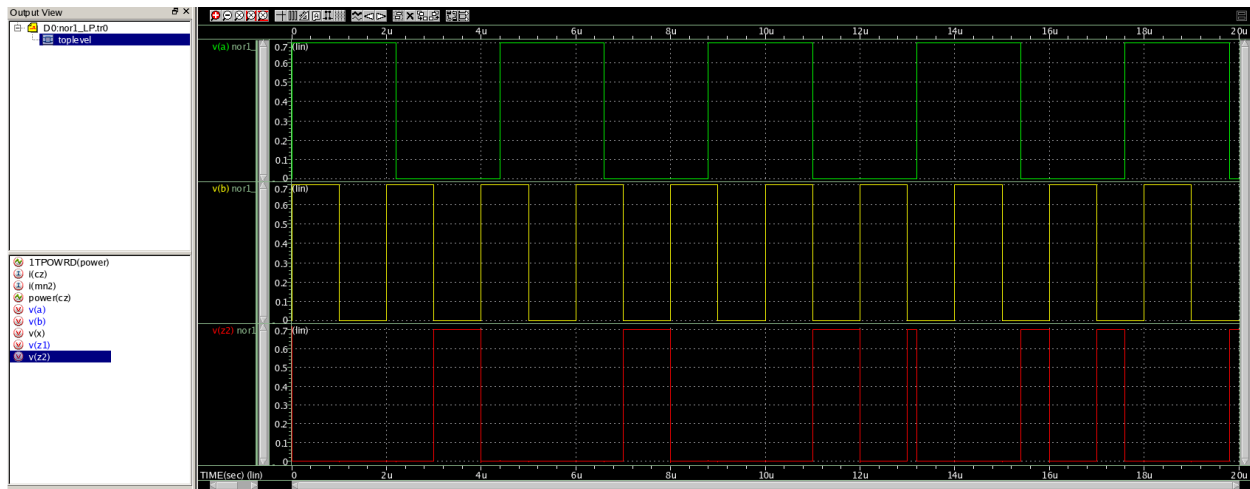

Waveform of NOR 1X LP

T_Fall_Delay = 4.1131 ps

T_Rise_Delay = 3.8257 ps

T_Fall_Time = 4.3760 ps

T_rise_Time =4.2590 ps

Switching power = -50.4293uW

Switching energy = 140.3077 aJ

Leakage current = 7.1383 pAmp

Leakage power = 4.9968 pW

NOR_LP_IG

```

1 *****
2 * lab3---1X_nor_IG_LP
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 6*number_fin
16 .param n_fin = 2*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z2 A X B pfet L=lg NFIN=p_fin
24 mn1 Z2 A 0 0 nfet L=lg NFIN=n_fin
25 mn2 Z2 B 0 0 nfet L=lg NFIN=n_fin
26
27 *add cap
28 Cz Z2 Gnd 'LoadCap'
29
30 *add voltage source
31 VX X 0 'vdd'
32
33 VA A 0 PULSE(0 0.7 0 10p 10p 1.2u 2.2u)
34 VB B 0 PULSE(0 0.7 0 10p 10p 0.5u 1.1u)
35
36 *define the initial condition of V(Z)
37 .IC V(Z2)='vdd'
38
39 *do transient analysis
40 *syntax: .TRAN tiner tstop START=stval
41 *tiner - time step
42 *tstop - final time
43 *stval - initial time (default 0)
44 .tran 0.1u 20u

```

```

44 .tran 0.1u 20u
45
46 *print the V(Z) to waveform file *.tr0
47 .print V(Z1)
48 .print V(Z2)
49 .print V(X)
50 .print V(A)
51 .print V(B)
52 .print i(Cz)
53 .print power(Cz)
54
55 *simulation options (you can modify this. Post is needed for .tran analysis)
56 .OPTION Post Brief NoMod probe measout
57
58 *measurement
59 .measure tran t_fall_delay_B TRIG V(B) VAL = 0.35
60 + RISE = 3 TARG V(Z2) VAL = 0.35 FALL = 2
61
62 .measure tran t_rise_delay_A TRIG V(A) VAL = 0.35
63 + FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 2
64
65 *.measure tran t_rise_delay_B TRIG V(B) VAL = 0.35 TD = 1n
66 *+ FALL = 2 TARG V(Z2) VAL = 0.35 RISE = 1
67
68 .measure tran t_fall_time TRIG V(Z2) VAL = 0.56 TD = 1n
69 + FALL = 2 TARG V(Z2) VAL = 0.14 FALL = 2
70
71 .measure tran t_rise_time TRIG V(Z2) VAL = 0.14 TD = 1n
72 + RISE = 2 TARG V(Z2) VAL = 0.56 RISE = 2
73
74 .measure tran time1 when V(Z2)=0.14
75 .measure tran time2 when V(Z2)=0.56
76 .measure tran switching_power AVG p(Cz) from 'time1' to 'time2'
77 .measure switching_energy param = 'abs(switching_power * (time2-time1))'
78
79
80 .measure tran leakage_current AVG i(mn2) from 1u to 2u
81 .measure leakage_power param = 'abs(vdd * leakage_current)'
82
83 .end

```

HSPICE Command of NOR 1X LP_IG

PFIN = 6, NFIN = 2


```

y
t_fall_delay_b= 3.4841p targ= 2.2000u trig= 2.2000u
t_rise_delay_a= 3.8528p targ= 3.4000u trig= 3.4000u
t_fall_time= 4.1207p targ= 4.4000u trig= 4.4000u
t_rise_time= 4.9263p targ= 3.4000u trig= 3.4000u
time1= 9.8130p
time2= 6.7983p
switching_power= -50.2411u from= 6.7983p to= 9.8130p
switching_energy= 151.4615a
leakage_current= 63.5980u from= 1.0000u to= 2.0000u
leakage_power= 44.5186u

```

***** job concluded

Time Details of NOR 1X LP_IG

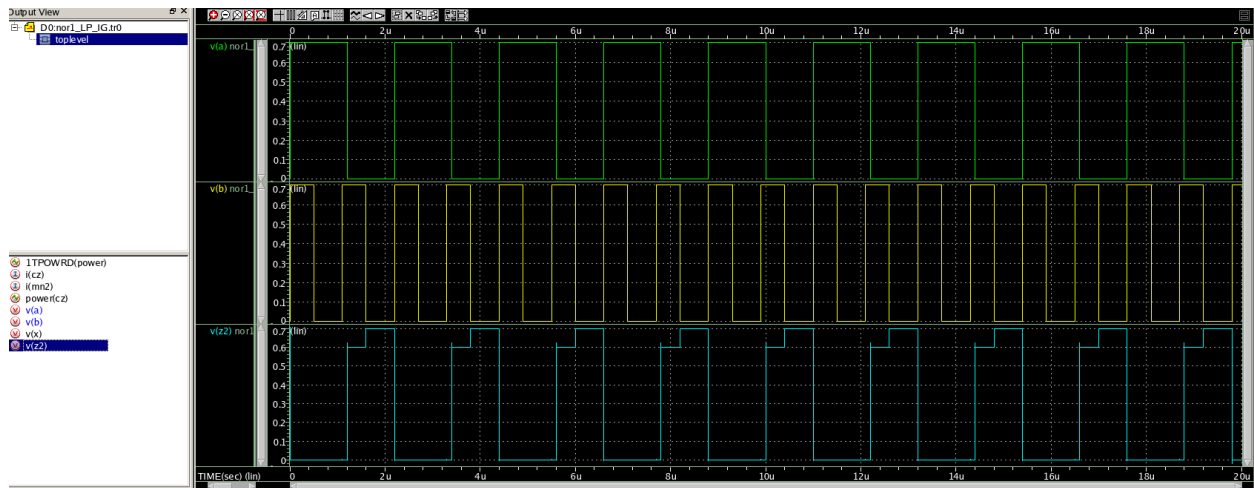

Waveform of NOR 1X LP_IG

T_Fall_Delay = 3.4841 ps

T_Rise_Delay = 3.8528 ps

T_Fall_Time = 4.1207 ps

T_rise_Time =4.9263 ps

Switching power = -50.2411 uW

Switching energy = 151.4615 aJ

Leakage current = 63.5980 uAmp

Leakage power = 44.5186 uW

1_BIT_Full_Adder

```

1 *****
2 * lab3---1Bit_Full_Adder
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param number_fin = 1
15 .param p_fin = 1*number_fin
16 .param n_fin = 1*number_fin
17 .param LoadCap = 1f
18
19 VSS Gnd 0 'vss'
20
21
22 *add transistors
23 mp1 Z1 A X A pfet L=lg NFIN=p_fin
24 mp2 Z1 B X B pfet L=lg NFIN=p_fin
25 mp3 Z3 C Z1 C pfet L=lg NFIN=p_fin
26 mp4 Z3 B Z2 B pfet L=lg NFIN=p_fin
27 mp5 Z2 A X A pfet L=lg NFIN=p_fin
28
29 mn1 Z3 C Z5 C nfet L=lg NFIN=n_fin
30 mn2 Z3 B Z4 B nfet L=lg NFIN=n_fin
31 mn3 Z5 A 0 A nfet L=lg NFIN=n_fin
32 mn4 Z5 B 0 B nfet L=lg NFIN=n_fin
33 mn5 Z4 A 0 A nfet L=lg NFIN=n_fin
34
35 mp6 Z6 Z3 Z8 Z3 pfet L=lg NFIN=p_fin
36 mp7 Z8 A X A pfet L=lg NFIN=p_fin
37 mp8 Z8 B X B pfet L=lg NFIN=p_fin
38 mp9 Z8 C X C pfet L=lg NFIN=p_fin
39 mp10 Z12 A X A pfet L=lg NFIN=p_fin
40 mp11 Z11 B Z12 B pfet L=lg NFIN=p_fin
41 mp12 Z6 C Z11 C pfet L=lg NFIN=p_fin
42
43 mn6 Z6 Z3 Z7 Z3 nfet L=lg NFIN=n_fin
44 mn7 Z7 A 0 A nfet L=lg NFIN=n_fin

```

```

44 mn7 Z7 A 0 A nfet L=lg NFIN=n_fin
45 mn8 Z7 B 0 B nfet L=lg NFIN=n_fin
46 mn9 Z7 C 0 C nfet L=lg NFIN=n_fin
47 mn10 Z6 A Z9 A nfet L=lg NFIN=n_fin
48 mn11 Z9 B Z10 B nfet L=lg NFIN=n_fin
49 mn12 Z10 C 0 C nfet L=lg NFIN=n_fin
50
51 mp13 Cout Z3 X Z3 pfet L=lg NFIN=p_fin
52 mn13 Cout Z3 0 Z3 nfet L=lg NFIN=n_fin
53
54 mp14 Sum Z6 X Z6 pfet L=lg NFIN=p_fin
55 mn14 Sum Z6 0 Z6 nfet L=lg NFIN=n_fin
56
57 *add cap
58 Cz Sum Gnd 'LoadCap'
59 Cz1 Cout Gnd 'LoadCap'
60
61 *add voltage source
62 VX X 0 'vdd'
63
64 VA A 0 PULSE(0 0.7 0 10p 10p 4.5u 9u)
65 VB B 0 PULSE(0 0.7 0 10p 10p 2.2u 4.2u)
66 VC C 0 PULSE(0 0.7 0 10p 10p 1u 2u)
67
68 *define the initial condition of V(Z)
69 .IC V(Sum)='vdd'
70 .IC V(Cout)='vdd'
71
72 *do transient analysis
73     *syntax: .TRAN tiner tstop START=stval
74     *tiner - time step
75     *tstop - final time
76     *stval - initial time (default 0)
77 .tran 0.1u 30u
78
79 *print the V(Z) to waveform file *.tr0
80 .print V(Sum)
81 .print V(Cout)
82 .print V(X)
83 .print V(A)
84 .print V(B)
85 .print V(C)
86 .print i(Cz)

```

```

79 *print the V(Z) to waveform file *.tr0
80 .print V(Sum)
81 .print V(Cout)
82 .print V(X)
83 .print V(A)
84 .print V(B)
85 .print V(C)
86 .print i(Cz)
87 .print power(Cz)
88
89 *simulation options (you can modify this. Post is needed for .tran analysis)
90 .OPTION Post Brief NoMod probe measout
91
92 *measurement
93 .measure tran t_fall_delay_Cout TRIG V(B) VAL = 0.35 TD = 1n
94 + RISE = 4 TARG V(Cout) VAL = 0.35 FALL = 7
95
96 .measure tran t_fall_delay_Sum TRIG V(C) VAL = 0.35 TD = 1n
97 + RISE = 2 TARG V(Sum) VAL = 0.35 FALL = 3
98
99 .measure tran t_rise_delay_Cout TRIG V(C) VAL = 0.35 TD = 1n
100 + FALL = 2 TARG V(Cout) VAL = 0.35 RISE = 1
101
102 .measure tran t_rise_delay_Sum TRIG V(C) VAL = 0.35 TD = 1n
103 + FALL = 2 TARG V(Sum) VAL = 0.35 RISE = 2
104
105 .measure tran t_fall_time_Cout TRIG V(Cout) VAL = 0.56 TD = 1n
106 + FALL = 2 TARG V(Cout) VAL = 0.14 FALL = 2
107
108 .measure tran t_rise_time_Cout TRIG V(Cout) VAL = 0.14 TD = 1n
109 + RISE = 2 TARG V(Cout) VAL = 0.56 RISE = 2
110
111 .measure tran t_fall_time_Sum TRIG V(Sum) VAL = 0.56 TD = 1n
112 + FALL = 2 TARG V(Sum) VAL = 0.14 FALL = 2
113
114 .measure tran t_rise_time_Sum TRIG V(Sum) VAL = 0.14 TD = 1n
115 + RISE = 2 TARG V(Sum) VAL = 0.56 RISE = 2
116
117 .end

```

HSPICE File of 1_Bit_Adder

PFIN = 1, NFIN = 1

```

t_fall_delay_cout= 200.0213n  targ= 17.0000u  trig= 16.8000u
t_fall_delay_sum= 13.1167p  targ= 4.0000u  trig= 4.0000u
t_rise_delay_cout= 1.0000u  targ= 4.0000u  trig= 3.0000u
t_rise_delay_sum= 14.6975p  targ= 3.0000u  trig= 3.0000u
t_fall_time_cout= 7.3886p  targ= 5.0000u  trig= 5.0000u
t_rise_time_cout= 8.1876p  targ= 6.0000u  trig= 6.0000u
t_fall_time_sum= 6.9551p  targ= 2.2000u  trig= 2.2000u
t_rise_time_sum= 7.9708p  targ= 3.0000u  trig= 3.0000u

```

***** job concluded

Time Details of 1 Bit Adder



Waveform of 1 Bit Full Adder

T_Fall_Delay = 13.117 ps

T_Rise_Delay = 14.6975 ps

COUT_T_Fall_Time = 7.3886 ps

COUT_T_rise_Time = 8.1876 ps

SUM_T_Fall_Time = 6.9551 ps

SUM_T_rise_Time = 7.9708 ps

Verification

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Hence all the values are verified, and the result is checked to receive a positive correlation.

Conclusion

The Hspice files of all the respective Compound gates were successfully designed using HSPICE command and the time delays and the rise and fall times were calculated and the logic was verified using the waveform.

Simple DRAM Simulation in HSPICE

```
1 *****
2 * lab3 sample hspice
3 *****
4
5 .include './hp7nfet.pm'
6 .include './hp7pfet.pm'
7
8 *define parameters
9 .param vdd=0.7
10 .param vss=0
11 .param fin_height=18n
12 .param fin_width=7n
13 .param lg=11n
14 .param p_fin = 1
15
16 VSS Gnd 0 'vss'
17
18 .param LoadCap = 1f
19
20 *name drain frontgate source backgate
21 *add transistors
22 mp1 Z vdd X vdd pfet L=lg NFIN=p_fin
23
24 *add cap
25 Cz Z Gnd 'LoadCap'
26
27 *add voltage source
28 VX X 0 'vdd/2'
29 VY Y 0 'vdd'
30
31 *define the initial condition of V(Z)
32 .IC V(Z)='vdd'
33
34 *do transient analysis
35     *syntax: .TRAN tiner tstop START=stval
36     *tiner - time step
37     *tstop - final time
38     *stval - initial time (default 0)
39 .tran 0.5m 2050m SWEEP data=table
40
41 .data table
42 p_fin LoadCap
43 1      1f
44 2      1f
```

```

41 .data table
42 p_fin LoadCap
43 1      1f
44 2      1f
45 3      1f
46 4      1f
47 5      1f
48 *50000^0.1 = 2.9505
49 1      2.9505f
50 2      2.9505f
51 3      2.9505f
52 4      2.9505f
53 5      2.9505f
54 *50000^0.2 = 8.70551
55 1      8.70551f
56 2      8.70551f
57 3      8.70551f
58 4      8.70551f
59 5      8.70551f
60 *50000^0.3 = 25.6857
61 1      25.6857f
62 2      25.6857f
63 3      25.6857f
64 4      25.6857f
65 5      25.6857f
66 *50000^0.4 = 75.7858
67 1      75.7858f
68 2      75.7858f
69 3      75.7858f
70 4      75.7858f
71 5      75.7858f
72 *50000^0.5 = 223.607
73 1      223.607f
74 2      223.607f
75 3      223.607f
76 4      223.607f
77 5      223.607f
78 *50000^0.6 = 659.754
79 1      659.754f
80 2      659.754f
81 3      659.754f
82 4      659.754f
83 5      659.754f

```

```

84 *50000^0.7 = 1946.61
85 1      1946.61f
86 2      1946.61f
87 3      1946.61f
88 4      1946.61f
89 5      1946.61f
90 *50000^0.8 = 5743.49
91 1      5743.49f
92 2      5743.49f
93 3      5743.49f
94 4      5743.49f
95 5      5743.49f
96 *50000^0.9 = 16946.2
97 1      16946.2f
98 2      16946.2f
99 3      16946.2f
100 4      16946.2f
101 5      16946.2f
102 *50000^1.0 = 50000
103 1      50000f
104 2      50000f
105 3      50000f
106 4      50000f
107 5      50000f
108
109
110 *print the V(Z) to waveform file *.tr0
111 *.print V(X)
112 *.print V(Y)
113 .print V(Z)
114
115 *simulation options (you can modify this. Post is needed for .tran analysis)
116 .OPTION Post Brief NoMod probe measout
117
118 *measurement --> These are samples of measurements. Modify as per your requirement.
119 .measure tran RTL TRIG AT=0 TARG v(Z) VAL=0.355 FALL=1
120 .measure tran avg_current AVG I(Cz) from 0 to 'RTL'
121 .measure tran avg_power AVG p(Cz)
122
123
124
125 .end

```

HSPICE Command of 1T DRAM Cell using Fin FET


```

1 *****
2 * lab3 sample hspice
3 *****
4
5 .include './lp32nm.pm'
6
7 *define parameters
8 .param vdd=1.0
9 .param vss=0
10 .param multiplier = 1
11 .param wd=120n*multiplier
12 .param lg=32n
13
14 VSS Gnd 0 'vss'
15
16 .param LoadCap = 1f
17
18 *name drain frontgate source backgate
19 *add transistors
20 mp1 Z vdd X vdd pmos L=lg W=wd
21
22 *add cap
23 Cz Z Gnd 'LoadCap'
24
25 *add voltage source
26 VX X 0 'vdd/2'
27 VY Y 0 'vdd'
28
29 *define the initial condition of V(Z)
30 .IC V(Z)='vdd'
31
32 *do transient analysis
33 *syntax: .TRAN tiner tstop START=stval
34 *tiner - time step
35 *tstop - final time
36 *stval - initial time (default 0)
37 .tran 0.5m 7550m SWEEP data=table
38
39 .data table
40 multiplier LoadCap
41 1 1f
42 2 1f
43 3 1f
44 4 1f

```

```

40 multiplier loadcap
41 1 1f
42 2 1f
43 3 1f
44 4 1f
45 5 1f
46 6 1f
47 7 1f
48 8 1f
49 9 1f
50 10 1f
51 11 1f
52 12 1f
53 13 1f
54 14 1f
55 15 1f
56 16 1f
57 *50000^0.1 = 2.9505
58 1 2.9505f
59 2 2.9505f
60 3 2.9505f
61 4 2.9505f
62 5 2.9505f
63 6 2.9505f
64 7 2.9505f
65 8 2.9505f
66 9 2.9505f
67 10 2.9505f
68 11 2.9505f
69 12 2.9505f
70 13 2.9505f
71 14 2.9505f
72 15 2.9505f
73 16 2.9505f
74 *50000^0.2 = 8.70551
75 1 8.70551f
76 2 8.70551f
77 3 8.70551f
78 4 8.70551f
79 5 8.70551f
80 6 8.70551f
81 7 8.70551f
82 8 8.70551f
83 9 8.70551f

```

76	2	8.70551f
77	3	8.70551f
78	4	8.70551f
79	5	8.70551f
80	6	8.70551f
81	7	8.70551f
82	8	8.70551f
83	9	8.70551f
84	10	8.70551f
85	11	8.70551f
86	12	8.70551f
87	13	8.70551f
88	14	8.70551f
89	15	8.70551f
90	16	8.70551f
91	$*50000^{0.3} = 25.6857$	
92	1	25.6857f
93	2	25.6857f
94	3	25.6857f
95	4	25.6857f
96	5	25.6857f
97	6	25.6857f
98	7	25.6857f
99	8	25.6857f
100	9	25.6857f
101	10	25.6857f
102	11	25.6857f
103	12	25.6857f
104	13	25.6857f
105	14	25.6857f
106	15	25.6857f
107	16	25.6857f
108	$*50000^{0.4} = 75.7858$	
109	1	75.7858f
110	2	75.7858f
111	3	75.7858f
112	4	75.7858f
113	5	75.7858f
114	6	75.7858f
115	7	75.7858f
116	8	75.7858f
117	9	75.7858f
118	10	75.7858f
119	11	75.7858f

118	10	75.7858f
119	11	75.7858f
120	12	75.7858f
121	13	75.7858f
122	14	75.7858f
123	15	75.7858f
124	16	75.7858f
125	$*50000^{0.5} = 223.607$	
126	1	223.607f
127	2	223.607f
128	3	223.607f
129	4	223.607f
130	5	223.607f
131	6	223.607f
132	7	223.607f
133	8	223.607f
134	9	223.607f
135	10	223.607f
136	11	223.607f
137	12	223.607f
138	13	223.607f
139	14	223.607f
140	15	223.607f
141	16	223.607f
142	$*50000^{0.6} = 659.754$	
143	1	659.754f
144	2	659.754f
145	3	659.754f
146	4	659.754f
147	5	659.754f
148	6	659.754f
149	7	659.754f
150	8	659.754f
151	9	659.754f
152	10	659.754f
153	11	659.754f
154	12	659.754f
155	13	659.754f
156	14	659.754f
157	15	659.754f
158	16	659.754f
159	$*50000^{0.7} = 1946.61$	
160	1	1946.61f
161	2	1946.61f

160	1	1946.61f
161	2	1946.61f
162	3	1946.61f
163	4	1946.61f
164	5	1946.61f
165	6	1946.61f
166	7	1946.61f
167	8	1946.61f
168	9	1946.61f
169	10	1946.61f
170	11	1946.61f
171	12	1946.61f
172	13	1946.61f
173	14	1946.61f
174	15	1946.61f
175	16	1946.61f
176	$*50000^{0.8} = 5743.49$	
177	1	5743.49f
178	2	5743.49f
179	3	5743.49f
180	4	5743.49f
181	5	5743.49f
182	6	5743.49f
183	7	5743.49f
184	8	5743.49f
185	9	5743.49f
186	10	5743.49f
187	11	5743.49f
188	12	5743.49f
189	13	5743.49f
190	14	5743.49f
191	15	5743.49f
192	16	5743.49f
193	$*50000^{0.9} = 16946.2$	
194	1	16946.2f
195	2	16946.2f
196	3	16946.2f
197	4	16946.2f
198	5	16946.2f
199	6	16946.2f
200	7	16946.2f
201	8	16946.2f
202	9	16946.2f
203	10	16946.2f

```

200 7      16946.2f
201 8      16946.2f
202 9      16946.2f
203 10     16946.2f
204 11     16946.2f
205 12     16946.2f
206 13     16946.2f
207 14     16946.2f
208 15     16946.2f
209 16     16946.2f
210 *50000^1.0 = 50000
211 1      50000f
212 2      50000f
213 3      50000f
214 4      50000f
215 5      50000f
216 6      50000f
217 7      50000f
218 8      50000f
219 9      50000f
220 10     50000f
221 11     50000f
222 12     50000f
223 13     50000f
224 14     50000f
225 15     50000f
226 16     50000f
227
228 *print the V(Z) to waveform file *.tr0
229 *.print V(X)
230 *.print V(Y)
231 .print V(Z)
232
233 *simulation options (you can modify this. Post is needed for .tran analysis)
234 .OPTION Post Brief NoMod probe measout
235
236 *measurement --> These are samples of measurements. Modify as per your requirement.
237 .measure tran RTL TRIG AT=0 TARG v(Z) VAL=0.55 FALL=1
238 .measure tran avg_current AVG I(Cz) from 0 to 'RTL'
239 .measure tran avg_power AVG p(Cz)
240
241 .end

```

HSPICE Command of 1T DRAM using MOS

After running the HSPICE files of the FinFet being designed using Fin Fet and MOS, we receive the .mt0 file. In order to automate the process and the draw the graph, we read the mt0 file and generate a list of data to be fed into matlab to plot the desired output.

Below is the python code which I used to extract the datas from the .mto file and pass on to the matlab code.

```
f = open("./DRAM_Sweep.mt0", "r")
a = f.read()
b=a.split('\n')
#print(len(b))
pfin=[]
loadcap=[]
rtl=[]
avg_current=[]
avg_power=[]

for i in range(0,len(b)-1,3):
    if(i>4):
        #print(i,b[i-1])
        list=[]
        t=b[i-1].split(" ")
        for i1 in t:
            if(i1):
                list.append(i1)
        pfin.append(list[1])
        loadcap.append(list[2])
        rtl.append(list[3])

        list1=[]
        #print(b[i])
        t1=b[i].split(" ")
        for j in t1:
            if (j):
                list1.append(j)
        avg_current.append(list1[0])
        avg_power.append(list1[1])
#print ("avg_current array", avg_current)
```

```

        list.append(i1)
    pfin.append(list[1])
    loadcap.append(list[2])
    rtl.append(list[3])

    list1=[]
    #print(b[i])
    t1=b[i].split(" ")
    for j in t1:
        if (j):
            list1.append(j)
            avg_current.append(list1[0])
            avg_power.append(list1[1])
#print ("avg_current array", avg_current)
#print('\n')
#print ("Pfin array " , pfin)
#print('\n')
#print ("Loadcap array", loadcap)
#print('\n')
#print ("avg_power array", avg_power)
#print('\n')
#print ("rtl array", rtl)

f=open("dram_finfet.txt","w")
f1=open("dram_finfet.csv","w")
f.write("pfin,avg_current,loadcap,avg_power,rtl\n")
f1.write("pfin,avg_current,loadcap,avg_power,rtl\n")
for i in range(len(pfin)):
    f.write(str(pfin[i])+","+str(avg_current[i])+','+str(loadcap[i])+","+str(avg_power[i])+','+str(rtl[i])+'\n')
    f1.write(str(pfin[i])+","+str(avg_current[i])+','+str(loadcap[i])+","+str(avg_power[i])+','+str(rtl[i])+'\n')
f.close()
f1.close()

```

Python code to make the input file for matlab plot – Fin Fet


```

f = open("./DRAM_MOSFET_Sweep.mt0", "r")
a = f.read()
b=a.split('\n')
#print(len(b))
multiplier=[]
loadcap_mos=[]
rtl_mos=[]
avg_current_mos=[]
avg_power_mos=[]

for i in range(0,len(b)-1,3):
    if(i>4):
        #print(i,b[i-1])
        list=[]
        t=b[i-1].split(" ")
        for i1 in t:
            if(i1):
                list.append(i1)
        multiplier.append(list[1])
        loadcap_mos.append(list[2])
        rtl_mos.append(list[3])

        list1=[]
        #print(b[i])
        t1=b[i].split(" ")
        for j in t1:
            if (j):
                list1.append(j)
        avg_current_mos.append(list1[0])
        avg_power_mos.append(list1[1])
print ("avg_current_Mosfet array", avg_current_mos)
print('\n')
print ("Multiplier array " . multiplier)

```

```

multiplier.append(list[1])
loadcap_mos.append(list[2])
rtl_mos.append(list[3])

list1=[]
#print(b[i])
t1=b[i].split(" ")
for j in t1:
    if (j):
        list1.append(j)
avg_current_mos.append(list1[0])
avg_power_mos.append(list1[1])
print ("avg_current_Mosfet array", avg_current_mos)
print('\n')
print ("Multiplier array " , multiplier)
print('\n')
print ("loadcap_Mosfet array", loadcap_mos)
print('\n')
print ("avg_power_Mosfet array", avg_power_mos)
print('\n')
print ("rtl_Mosfet array", rtl_mos)

f=open("mosfet_finfet.txt","w")
f1=open("mosfet_finfet.csv","w")
f.write("multiplier,avg_current,loadcap,avg_power,rtl\n")
f1.write("multiplier,avg_current,loadcap,avg_power,rtl\n")
print(len(multiplier))
for i in range(len(multiplier)):
    f.write(str(multiplier[i])+","+str(avg_current_mos[i])+","+str(loadcap_mos[i])+","+str(avg_power_mos[i])+","+str(rtl_mos[i])+'\n')
    f1.write(str(multiplier[i])+","+str(avg_current_mos[i])+","+str(loadcap_mos[i])+","+str(avg_power_mos[i])+","+str(rtl_mos[i])+'\n')
f.close()
f1.close()

```

Python code to make the input file for matlab plot – MOS

After running the above file, we are generating the .text file, which is being used to feed to the matlab, as well as we use the data to find the asked statistics of the DRAM File.

```

from statistics import stdev
from statistics import mean

file = open("./DRAM_Sweep.mt0", "r")
file1= open("./DRAM_MOSFET_Sweep.mt0", "r")
data = file.read()
data1 = file1.read()
b=data.split('\n')
b1=data.split('\n')
p_fin = []
mul = []
avg_current = []
avg_current_mos = []
loadcap = []
loadcap_mos = []
avg_power = []
avg_power_mos = []
rtl = []
rtl_mos = []

for i in range(0, len(b)-1, 3):
    if(i > 4):
        #print (b[i-1])
        list = []
        temp1 = b[i-1].split(" ")
        for var in temp1:
            if(var):
                list.append(float(var))
        p_fin.append(list[1])
        loadcap.append(list[2])
        rtl.append(list[3])

```

```

    p_line.append(list[1])
    loadcap.append(list[2])
    rtl.append(list[3])

    #i
    list1 = []
    temp1 = b[i].split(" ")
    for var in temp1:
        if(var):
            list1.append(float(var))
    #print (list)
    avg_current.append(list1[0])
    avg_power.append(list1[1])

print("Maximum value of RTL "+str(max(rtl)))
print("Minimum value of RTL "+str(min(rtl)))
print("Standard Deviation of RTL "+str(stdev(rtl)))
print("Average value of RTL "+str(mean(rtl)))
print("Average value of Average Current "+str(mean(avg_current)))
print("Maximum value of Average Current "+str(max(avg_current)))
print("Minimum value of Average Current "+str(min(avg_current)))
print("Standard Deviation of Average Current "+str(stdev(avg_current)))
print("Maximum value of average power "+str(max(avg_power)))
print("Minimum value of average power "+str(min(avg_power)))
print("Standard Deviation of average power "+str(stdev(avg_power)))
print("Average value of average power "+str(mean(avg_power)))

for i in range(0, len(b1)-1, 3):
    if(i > 4):
        #print (b[i-1])
        list2 = []
        temp2 = b1[i-1].split(" ")

```

```

print (b[i-1])
list2 = []
temp2 = b1[i-1].split(" ")
for var1 in temp2:
    if(var1):
        list2.append(float(var1))
mul.append(list2[1])
loadcap_mos.append(list2[2])
rtl_mos.append(list2[3])

#i
list3 = []
temp3 = b[i].split(" ")
for var2 in temp3:
    if(var2):
        list3.append(float(var2))
#print (list)
avg_current_mos.append(list3[0])
avg_power_mos.append(list3[1])

print("Maximum value of RTL MOS "+str(max(rtl_mos)))
print("Minimum value of RTL MOS "+str(min(rtl_mos)))
print("Standard Deviation of RTL MOS "+str(stdev(rtl_mos)))
print("Average value of RTL MOS "+str(mean(rtl_mos)))
print("Average value of Average Current MOS "+str(mean(avg_current_mos)))
print("Maximum value of Average Current MOS "+str(max(avg_current_mos)))
print("Minimum value of Average Current MOS "+str(min(avg_current_mos)))
print("Standard Deviation of Average Current MOS "+str(stdev(avg_current_mos)))
print("Maximum value of average power MOS "+str(max(avg_power_mos)))
print("Minimum value of average power MOS "+str(min(avg_power_mos)))
print("Standard Deviation of average power MOS "+str(stdev(avg_power_mos)))
print("Average value of average power MOS "+str(mean(avg_power_mos)))

```

```
print("Standard Deviation of average power MOS"+str(stdev(avg_power_mos)))
print("Average value of average power MOS"+str(mean(avg_power_mos)))
```

```
Maximum value of RTL 0.007382
Minimum value of RTL 1.598e-08
Standard Deviation of RTL 0.0012369681126332022
Average value of RTL 0.00049078344
Average value of Average Current -6.695218181818182e-09
Maximum value of Average Current -1.122e-09
Minimum value of Average Current -5.206e-08
Standard Deviation of Average Current 7.517518443217e-09
Maximum value of average power -7.357e-17
Minimum value of average power -4.148e-12
Standard Deviation of average power 1.162797944700218e-12
Average value of average power -5.20267938e-13
Maximum value of RTL MOS 0.007382
Minimum value of RTL MOS 1.598e-08
Standard Deviation of RTL MOS 0.0012369681126332022
Average value of RTL MOS 0.00049078344
Average value of Average Current MOS -6.695218181818182e-09
Maximum value of Average Current MOS -1.122e-09
Minimum value of Average Current MOS -5.206e-08
Standard Deviation of Average Current MOS 7.517518443217e-09
Maximum value of average power MOS -7.357e-17
Minimum value of average power MOS -4.148e-12
Standard Deviation of average power MOS 1.162797944700218e-12
Average value of average power MOS -5.20267938e-13
```

Python Code and the Output Statistics Calculated.

The above diagrams are representing the python code and the statistics calculated for the DRAM, the obtained statistics are verified and the reported.

Below is the Matlab code and the further documentation of DRAM using FinFET

```

1 - input_data = importdata(strcat(pwd, './dram_finfet.txt'));
2 - Fin = input_data.data(:,1);
3 - Capacitance_FINFET = input_data.data(:,3);
4 - RTL_FINFET=input_data.data(:,5);
5 - avgcurrent_FINFET=input_data.data(:,2);
6 - avgPower_FINFET=input_data.data(:,4);
7
8 - AverageCurrent_FINFET=[];
9 - AveragePower_FINFET=[];
10 - RtlPlotFinfet=[];
11
12 - for i=1:11
13 -     RtlPlotFinfet=horzcat(RtlPlotFinfet,RTL_FINFET(1+5*(i-1):5*i));
14 -     AverageCurrent_FINFET=horzcat(AverageCurrent_FINFET,avgcurrent_FINFET(1+5*(i-1):5*i));
15 -     AveragePower_FINFET=horzcat(AveragePower_FINFET,avgPower_FINFET(1+5*(i-1):5*i));
16 - end
17
18 - figure
19 - surf(unique(Capacitance_FINFET),unique(Fin),RtlPlotFinfet)
20 - title('DRAM FINFET Refresh Time Limit Plot')
21 - xlabel('Capacitance_Load (fF)')
22 - ylabel('PFins')
23 - zlabel('RTL(sec)')
24
25 - figure
26 - surf(unique(Capacitance_FINFET),unique(Fin),AverageCurrent_FINFET)
27 - title('DRAM FINFET Average Current Plot')
28 - xlabel('Capacitance_Load (fF)')
29
30 - xlabel('Capacitance_Load (fF)')
31 - ylabel('Fins')
32 - zlabel('Average_Current (Amp)')
33
34 - figure
35 - surf(unique(Capacitance_FINFET),unique(Fin),AveragePower_FINFET)
36 - title('DRAM FINFET Average Power Plot')
37 - xlabel('Capacitance_Load (fF)')
38 - ylabel('Fins')
39 - zlabel('Average_Power (Watt)')

```

MATLAB code for DRAM_FinFet



dram_finfet.txt

Input to the MATLAB File


```

pfin,avg_current,loadcap,avg_power,rtl
1.0000,-1.947e-09,1.000e-15,-7.890e-17,1.589e-07
2.0000,-3.566e-09,1.000e-15,-8.191e-17,8.532e-08
3.0000,-4.740e-09,1.000e-15,-8.531e-17,5.497e-08
4.0000,-6.222e-09,1.000e-15,-7.357e-17,4.095e-08
5.0000,-1.923e-08,1.000e-15,-1.725e-16,1.598e-08
1.0000,-1.687e-09,2.951e-15,-1.973e-16,4.814e-07
2.0000,-3.273e-09,2.951e-15,-1.839e-16,2.350e-07
3.0000,-5.781e-09,2.951e-15,-2.330e-16,1.579e-07
4.0000,-7.318e-09,2.951e-15,-2.561e-16,1.239e-07
5.0000,-9.306e-09,2.951e-15,-2.563e-16,9.668e-08
1.0000,-1.710e-09,8.706e-15,-5.627e-16,1.366e-06
2.0000,-2.976e-09,8.706e-15,-5.395e-16,7.495e-07
3.0000,-5.013e-09,8.706e-15,-5.806e-16,4.779e-07
4.0000,-6.816e-09,8.706e-15,-5.662e-16,3.424e-07
5.0000,-7.906e-09,8.706e-15,-5.738e-16,2.919e-07
1.0000,-1.589e-09,2.569e-14,-1.593e-15,4.216e-06
2.0000,-3.442e-09,2.569e-14,-1.735e-15,2.062e-06
3.0000,-5.076e-09,2.569e-14,-1.661e-15,1.357e-06
4.0000,-6.174e-09,2.569e-14,-1.624e-15,1.100e-06
5.0000,-7.871e-09,2.569e-14,-1.574e-15,8.435e-07
1.0000,-1.887e-09,7.579e-14,-4.979e-15,1.128e-05
2.0000,-1.890e-08,7.579e-14,-6.833e-15,1.549e-06
3.0000,-4.943e-09,7.579e-14,-5.163e-15,4.385e-06
4.0000,-6.451e-09,7.579e-14,-5.021e-15,3.296e-06
5.0000,-9.844e-09,7.579e-14,-5.812e-15,2.368e-06
1.0000,-1.122e-09,2.236e-13,-1.095e-14,3.459e-05
2.0000,-3.683e-09,2.236e-13,-1.539e-14,1.755e-05
3.0000,-5.618e-09,2.236e-13,-1.467e-14,1.117e-05
4.0000,-2.186e-08,2.236e-13,-2.088e-14,3.955e-06
5.0000,-5.206e-08,2.236e-13,-2.049e-14,1.649e-06
1.0000,-1.676e-09,6.598e-13,-4.284e-14,1.053e-04
2.0000,-3.275e-09,6.598e-13,-3.971e-14,5.060e-05
3.0000,-3.390e-09,6.598e-13,-3.220e-14,3.360e-05
4.0000,-8.195e-09,6.598e-13,-4.734e-14,2.373e-05
5.0000,-9.337e-09,6.598e-13,-4.623e-14,2.071e-05
1.0000,-1.679e-09,1.947e-12,-1.213e-13,3.005e-04
2.0000,-3.472e-09,1.947e-12,-1.316e-13,1.539e-04
3.0000,-4.985e-09,1.947e-12,-1.263e-13,1.044e-04
4.0000,-6.825e-09,1.947e-12,-1.224e-13,7.406e-05
5.0000,-8.039e-09,1.947e-12,-1.194e-13,6.194e-05

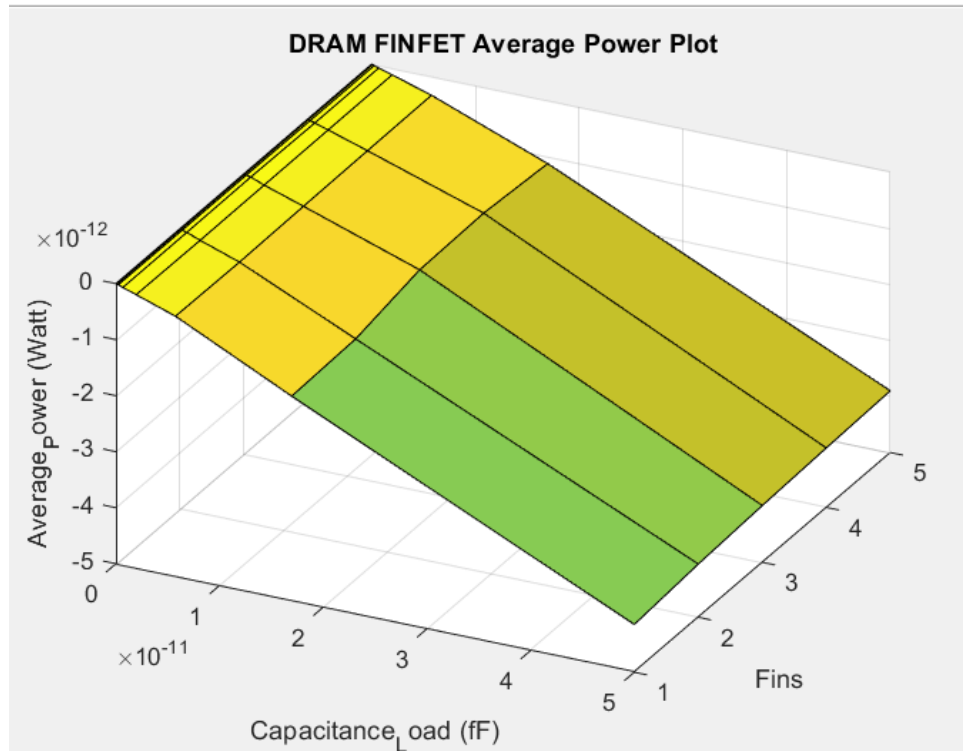
1.0000,-1.641e-09,5.743e-12,-3.589e-13,9.216e-04
2.0000,-3.374e-09,5.743e-12,-3.737e-13,4.574e-04
3.0000,-4.983e-09,5.743e-12,-3.575e-13,2.987e-04
4.0000,-5.964e-09,5.743e-12,-3.458e-13,2.457e-04
5.0000,-7.650e-09,5.743e-12,-3.367e-13,1.866e-04
1.0000,-2.068e-09,1.695e-11,-1.352e-12,2.618e-03
2.0000,-3.728e-09,1.695e-11,-1.310e-12,1.448e-03
3.0000,-4.881e-09,1.695e-11,-1.058e-12,9.134e-04
4.0000,-6.309e-09,1.695e-11,-1.026e-12,6.912e-04
5.0000,-8.966e-09,1.695e-11,-1.123e-12,5.107e-04
1.0000,-2.189e-09,5.000e-11,-4.148e-12,7.382e-03
2.0000,-4.078e-09,5.000e-11,-4.050e-12,3.949e-03
3.0000,-6.144e-09,5.000e-11,-3.986e-12,2.601e-03
4.0000,-7.555e-09,5.000e-11,-3.938e-12,2.118e-03
5.0000,-9.823e-09,5.000e-11,-3.899e-12,1.617e-03

```


Dram_finfet.txt Input Data Set to the matlab



DRAM FINFET Average Power Plot

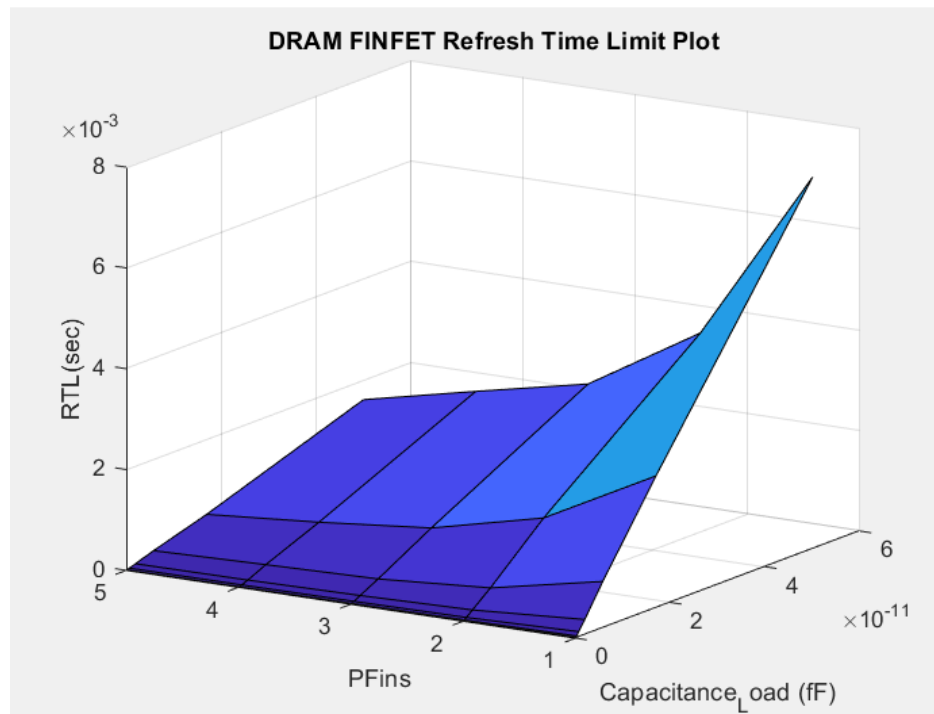

DRAM FINFET Refresh Time Limit Plot

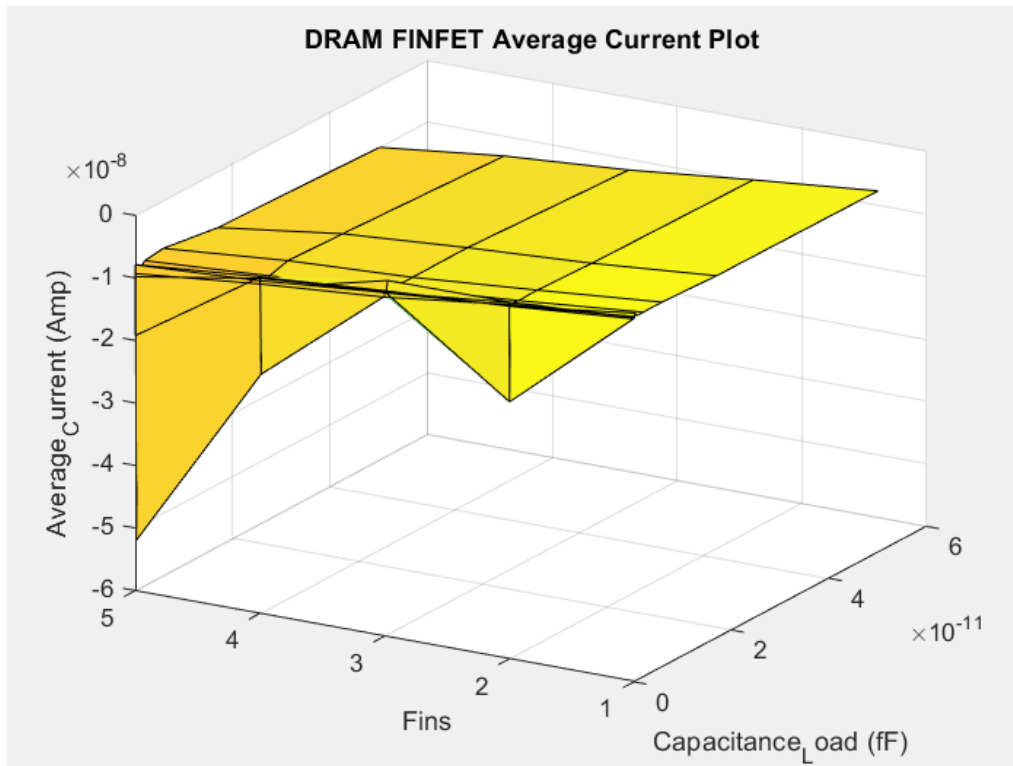

DRAM FINFET Average Current Plot

Below is the Matlab code and the further documentation of DRAM using Mos

```
1 - MOS_data = importdata(strcat(pwd, './mosfet_finfet.txt'));
2 - Multiplier = MOS_data.data(:,1);
3 - Cap_MOS = MOS_data.data(:,3);
4 - RTL_MOS=MOS_data.data(:,5);
5 - avg_I_MOS=MOS_data.data(:,2);
6 - avg_P_MOS=MOS_data.data(:,4);
7
8 - RTL_plot_MOS=[];
9 - I_avg_MOS=[];
10 - P_avg_MOS=[];
11
12 - for i=1:11
13 -     RTL_plot_MOS=horzcat(RTL_plot_MOS,RTL_MOS(1+16*(i-1):16*i));
14 -     I_avg_MOS=horzcat(I_avg_MOS,avg_I_MOS(1+16*(i-1):16*i));
15 -     P_avg_MOS=horzcat(P_avg_MOS,avg_P_MOS(1+16*(i-1):16*i));
16 - end
17
18 - figure
19 - surf(unique(Cap_MOS),unique(Multiplier),RTL_plot_MOS)
20 - title('DRAM MOS RTL Plot')
21 - xlabel('Capacitance Load (fF)')
22 - ylabel('Multiplier')
23 - zlabel('Refresh Time Limit (sec)')
24
25 - figure
26 - surf(unique(Cap_MOS),unique(Multiplier),I_avg_MOS)
27 - title('DRAM MOS Average Current Plot')
28 - xlabel('Capacitance Load (fF)')
29 - ylabel('Multiplier')
30 - zlabel('Average Current (Amp)')
31
32 - figure
33 - surf(unique(Cap_MOS),unique(Multiplier),P_avg_MOS)
34 - title('DRAM MOS Average Power Plot')
35 - xlabel('Capacitance Load (fF)')
36 - ylabel('Multiplier')
37 - zlabel('Average Power (Watt)')
```

MATLAB code for DRAM_Mos



mosfet_finfet.txt

Input to the MATLAB File

	multiplier	avg_current	loadcap	avg_power	rtl
1.0000	-7.493e-13	1.000e-15	-4.755e-17	5.340e-04	
2.0000	-7.445e-13	1.000e-15	-4.784e-17	5.422e-04	
3.0000	-6.940e-13	1.000e-15	-4.859e-17	5.828e-04	
4.0000	-6.398e-13	1.000e-15	-4.918e-17	6.363e-04	
5.0000	-5.911e-13	1.000e-15	-4.887e-17	6.940e-04	
6.0000	-5.555e-13	1.000e-15	-4.911e-17	7.404e-04	
7.0000	-5.279e-13	1.000e-15	-5.050e-17	7.797e-04	
8.0000	-5.052e-13	1.000e-15	-5.079e-17	8.149e-04	
9.0000	-4.847e-13	1.000e-15	-5.097e-17	8.501e-04	
10.0000	-4.613e-13	1.000e-15	-5.036e-17	8.973e-04	
11.0000	-4.433e-13	1.000e-15	-4.968e-17	9.364e-04	
12.0000	-4.282e-13	1.000e-15	-4.934e-17	9.707e-04	
13.0000	-4.153e-13	1.000e-15	-4.953e-17	1.002e-03	
14.0000	-4.041e-13	1.000e-15	-4.983e-17	1.030e-03	
15.0000	-3.941e-13	1.000e-15	-5.040e-17	1.056e-03	
16.0000	-3.852e-13	1.000e-15	-5.072e-17	1.081e-03	
1.0000	-1.163e-12	2.951e-15	-1.472e-16	1.035e-03	
2.0000	-1.443e-12	2.951e-15	-1.462e-16	8.342e-04	
3.0000	-1.427e-12	2.951e-15	-1.467e-16	8.477e-04	
4.0000	-1.365e-12	2.951e-15	-1.473e-16	8.875e-04	
5.0000	-1.299e-12	2.951e-15	-1.479e-16	9.334e-04	
6.0000	-1.213e-12	2.951e-15	-1.489e-16	1.009e-03	
7.0000	-1.151e-12	2.951e-15	-1.492e-16	1.067e-03	
8.0000	-1.102e-12	2.951e-15	-1.487e-16	1.116e-03	
9.0000	-1.062e-12	2.951e-15	-1.487e-16	1.158e-03	
10.0000	-1.029e-12	2.951e-15	-1.502e-16	1.195e-03	
11.0000	-9.999e-13	2.951e-15	-1.532e-16	1.229e-03	
12.0000	-9.740e-13	2.951e-15	-1.554e-16	1.260e-03	
13.0000	-9.477e-13	2.951e-15	-1.576e-16	1.296e-03	
14.0000	-9.164e-13	2.951e-15	-1.583e-16	1.346e-03	
15.0000	-8.897e-13	2.951e-15	-1.580e-16	1.389e-03	
16.0000	-8.671e-13	2.951e-15	-1.573e-16	1.427e-03	
1.0000	-1.459e-12	8.706e-15	-4.558e-16	2.500e-03	
2.0000	-2.315e-12	8.706e-15	-4.481e-16	1.555e-03	
3.0000	-2.591e-12	8.706e-15	-4.469e-16	1.396e-03	
4.0000	-2.631e-12	8.706e-15	-4.472e-16	1.380e-03	
5.0000	-2.585e-12	8.706e-15	-4.479e-16	1.408e-03	
6.0000	-2.520e-12	8.706e-15	-4.487e-16	1.444e-03	
7.0000	-2.447e-12	8.706e-15	-4.493e-16	1.485e-03	
8.0000	-2.361e-12	8.706e-15	-4.506e-16	1.541e-03	
9.0000	-2.255e-12	8.706e-15	-4.513e-16	1.625e-03	
10.0000	-2.169e-12	8.706e-15	-4.533e-16	1.695e-03	
11.0000	-2.099e-12	8.706e-15	-4.533e-16	1.754e-03	
12.0000	-2.045e-12	8.706e-15	-4.529e-16	1.801e-03	
13.0000	-1.996e-12	8.706e-15	-4.522e-16	1.844e-03	
14.0000	-1.952e-12	8.706e-15	-4.510e-16	1.883e-03	
15.0000	-1.913e-12	8.706e-15	-4.499e-16	1.919e-03	
16.0000	-1.878e-12	8.706e-15	-4.493e-16	1.953e-03	
1.0000	-1.603e-12	2.569e-14	-1.405e-15	6.938e-03	
2.0000	-2.901e-12	2.569e-14	-1.375e-15	3.771e-03	
3.0000	-3.848e-12	2.569e-14	-1.364e-15	2.821e-03	
4.0000	-4.345e-12	2.569e-14	-1.360e-15	2.500e-03	
5.0000	-4.588e-12	2.569e-14	-1.358e-15	2.372e-03	
6.0000	-4.668e-12	2.569e-14	-1.357e-15	2.336e-03	
7.0000	-4.660e-12	2.569e-14	-1.357e-15	2.343e-03	
8.0000	-4.608e-12	2.569e-14	-1.357e-15	2.370e-03	
9.0000	-4.539e-12	2.569e-14	-1.357e-15	2.406e-03	
10.0000	-4.472e-12	2.569e-14	-1.357e-15	2.441e-03	
11.0000	-4.394e-12	2.569e-14	-1.357e-15	2.480e-03	
12.0000	-4.319e-12	2.569e-14	-1.356e-15	2.519e-03	
13.0000	-4.250e-12	2.569e-14	-1.357e-15	2.554e-03	
14.0000	-4.108e-12	2.569e-14	-1.358e-15	2.658e-03	
15.0000	-3.988e-12	2.569e-14	-1.358e-15	2.749e-03	
16.0000	-3.885e-12	2.569e-14	-1.359e-15	2.830e-03	

1.0000, -1.697e-12, 7.579e-14, -4.273e-15, 1.975e-02
 2.0000, -3.260e-12, 7.579e-14, -4.199e-15, 1.014e-02
 3.0000, -4.555e-12, 7.579e-14, -4.159e-15, 7.227e-03
 4.0000, -5.730e-12, 7.579e-14, -4.135e-15, 5.707e-03
 5.0000, -6.631e-12, 7.579e-14, -4.121e-15, 4.918e-03
 6.0000, -7.232e-12, 7.579e-14, -4.111e-15, 4.515e-03
 7.0000, -7.658e-12, 7.579e-14, -4.105e-15, 4.265e-03
 8.0000, -7.939e-12, 7.579e-14, -4.100e-15, 4.114e-03
 9.0000, -8.099e-12, 7.579e-14, -4.096e-15, 4.033e-03
 10.0000, -8.173e-12, 7.579e-14, -4.094e-15, 3.998e-03
 11.0000, -8.182e-12, 7.579e-14, -4.091e-15, 3.996e-03
 12.0000, -8.151e-12, 7.579e-14, -4.089e-15, 4.013e-03
 13.0000, -8.093e-12, 7.579e-14, -4.085e-15, 4.043e-03
 14.0000, -8.023e-12, 7.579e-14, -4.083e-15, 4.078e-03
 15.0000, -7.943e-12, 7.579e-14, -4.082e-15, 4.119e-03
 16.0000, -7.858e-12, 7.579e-14, -4.080e-15, 4.162e-03
 1.0000, -1.708e-12, 2.236e-13, -1.277e-14, 5.871e-02
 2.0000, -3.375e-12, 2.236e-13, -1.268e-14, 2.951e-02
 3.0000, -4.932e-12, 2.236e-13, -1.259e-14, 2.010e-02
 4.0000, -6.420e-12, 2.236e-13, -1.252e-14, 1.536e-02
 5.0000, -7.866e-12, 2.236e-13, -1.248e-14, 1.247e-02
 6.0000, -9.107e-12, 2.236e-13, -1.244e-14, 1.075e-02
 7.0000, -1.010e-11, 2.236e-13, -1.241e-14, 9.689e-03
 8.0000, -1.099e-11, 2.236e-13, -1.239e-14, 8.901e-03
 9.0000, -1.178e-11, 2.236e-13, -1.237e-14, 8.300e-03
 10.0000, -1.246e-11, 2.236e-13, -1.235e-14, 7.837e-03
 11.0000, -1.298e-11, 2.236e-13, -1.233e-14, 7.512e-03
 12.0000, -1.344e-11, 2.236e-13, -1.232e-14, 7.244e-03
 13.0000, -1.380e-11, 2.236e-13, -1.231e-14, 7.051e-03
 14.0000, -1.405e-11, 2.236e-13, -1.230e-14, 6.917e-03
 15.0000, -1.425e-11, 2.236e-13, -1.229e-14, 6.819e-03
 16.0000, -1.434e-11, 2.236e-13, -1.228e-14, 6.773e-03

1.0000, -1.723e-12, 6.598e-13, -3.789e-14, 0.1725
 2.0000, -3.462e-12, 6.598e-13, -3.777e-14, 8.543e-02
 3.0000, -5.104e-12, 6.598e-13, -3.765e-14, 5.795e-02
 4.0000, -6.692e-12, 6.598e-13, -3.755e-14, 4.412e-02
 5.0000, -8.366e-12, 6.598e-13, -3.746e-14, 3.513e-02
 6.0000, -9.974e-12, 6.598e-13, -3.738e-14, 2.939e-02
 7.0000, -1.135e-11, 6.598e-13, -3.731e-14, 2.583e-02
 8.0000, -1.273e-11, 6.598e-13, -3.725e-14, 2.303e-02
 9.0000, -1.396e-11, 6.598e-13, -3.720e-14, 2.098e-02
 10.0000, -1.517e-11, 6.598e-13, -3.715e-14, 1.929e-02
 11.0000, -1.636e-11, 6.598e-13, -3.711e-14, 1.787e-02
 12.0000, -1.754e-11, 6.598e-13, -3.708e-14, 1.662e-02
 13.0000, -1.871e-11, 6.598e-13, -3.705e-14, 1.554e-02
 14.0000, -1.965e-11, 6.598e-13, -3.703e-14, 1.478e-02
 15.0000, -2.039e-11, 6.598e-13, -3.700e-14, 1.425e-02
 16.0000, -2.107e-11, 6.598e-13, -3.696e-14, 1.379e-02
 1.0000, -1.748e-12, 1.947e-12, -1.120e-13, 0.5009
 2.0000, -3.490e-12, 1.947e-12, -1.119e-13, 0.2507
 3.0000, -5.163e-12, 1.947e-12, -1.118e-13, 0.1698
 4.0000, -6.860e-12, 1.947e-12, -1.117e-13, 0.1277
 5.0000, -8.558e-12, 1.947e-12, -1.116e-13, 0.1022
 6.0000, -1.030e-11, 1.947e-12, -1.114e-13, 8.471e-02
 7.0000, -1.200e-11, 1.947e-12, -1.113e-13, 7.258e-02
 8.0000, -1.354e-11, 1.947e-12, -1.112e-13, 6.440e-02
 9.0000, -1.503e-11, 1.947e-12, -1.111e-13, 5.804e-02
 10.0000, -1.648e-11, 1.947e-12, -1.110e-13, 5.294e-02
 11.0000, -1.795e-11, 1.947e-12, -1.109e-13, 4.859e-02
 12.0000, -1.944e-11, 1.947e-12, -1.108e-13, 4.480e-02
 13.0000, -2.094e-11, 1.947e-12, -1.107e-13, 4.153e-02
 14.0000, -2.243e-11, 1.947e-12, -1.107e-13, 3.871e-02
 15.0000, -2.394e-11, 1.947e-12, -1.106e-13, 3.620e-02
 16.0000, -2.534e-11, 1.947e-12, -1.106e-13, 3.417e-02


```

1.0000,-1.728e-12,5.743e-12,-3.300e-13,1.4975
2.0000,-3.476e-12,5.743e-12,-3.304e-13,0.7438
3.0000,-5.222e-12,5.743e-12,-3.303e-13,0.4948
4.0000,-6.911e-12,5.743e-12,-3.302e-13,0.3744
5.0000,-8.594e-12,5.743e-12,-3.301e-13,0.3013
6.0000,-1.031e-11,5.743e-12,-3.300e-13,0.2510
7.0000,-1.205e-11,5.743e-12,-3.298e-13,0.2146
8.0000,-1.379e-11,5.743e-12,-3.297e-13,0.1872
9.0000,-1.561e-11,5.743e-12,-3.295e-13,0.1652
10.0000,-1.720e-11,5.743e-12,-3.294e-13,0.1501
11.0000,-1.879e-11,5.743e-12,-3.293e-13,0.1374
12.0000,-2.035e-11,5.743e-12,-3.292e-13,0.1270
13.0000,-2.185e-11,5.743e-12,-3.291e-13,0.1183
14.0000,-2.341e-11,5.743e-12,-3.290e-13,0.1104
15.0000,-2.499e-11,5.743e-12,-3.289e-13,0.1034
16.0000,-2.662e-11,5.743e-12,-3.288e-13,9.699e-02
1.0000,-1.726e-12,1.695e-11,-9.415e-13,4.4184
2.0000,-3.465e-12,1.695e-11,-9.702e-13,2.2013
3.0000,-5.180e-12,1.695e-11,-9.739e-13,1.4743
4.0000,-6.927e-12,1.695e-11,-9.743e-13,1.1018
5.0000,-8.624e-12,1.695e-11,-9.745e-13,0.8855
6.0000,-1.044e-11,1.695e-11,-9.745e-13,0.7306
7.0000,-1.213e-11,1.695e-11,-9.745e-13,0.6292
8.0000,-1.379e-11,1.695e-11,-9.745e-13,0.5539
9.0000,-1.548e-11,1.695e-11,-9.744e-13,0.4934
10.0000,-1.721e-11,1.695e-11,-9.744e-13,0.4438
11.0000,-1.899e-11,1.695e-11,-9.743e-13,0.4018
12.0000,-2.082e-11,1.695e-11,-9.743e-13,0.3660
13.0000,-2.253e-11,1.695e-11,-9.742e-13,0.3382
14.0000,-2.414e-11,1.695e-11,-9.742e-13,0.3160
15.0000,-2.576e-11,1.695e-11,-9.743e-13,0.2964
16.0000,-2.739e-11,1.695e-11,-9.744e-13,0.2787

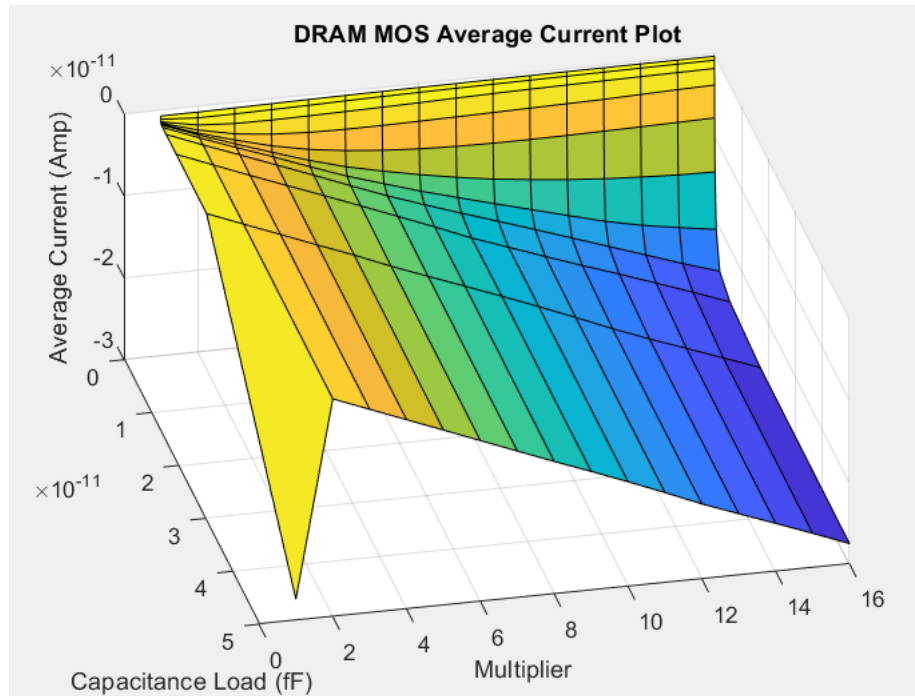
1.0000,-2.739e-11,5.000e-11,-2.380e-12,8.4228
2.0000,-3.450e-12,5.000e-11,-2.670e-12,6.5208
3.0000,-5.186e-12,5.000e-11,-2.781e-12,4.3380
4.0000,-6.914e-12,5.000e-11,-2.830e-12,3.2548
5.0000,-8.643e-12,5.000e-11,-2.853e-12,2.6038
6.0000,-1.038e-11,5.000e-11,-2.863e-12,2.1675
7.0000,-1.212e-11,5.000e-11,-2.869e-12,1.8568
8.0000,-1.385e-11,5.000e-11,-2.872e-12,1.6250
9.0000,-1.552e-11,5.000e-11,-2.873e-12,1.4517
10.0000,-1.724e-11,5.000e-11,-2.874e-12,1.3073
11.0000,-1.902e-11,5.000e-11,-2.874e-12,1.1842
12.0000,-2.087e-11,5.000e-11,-2.875e-12,1.0777
13.0000,-2.252e-11,5.000e-11,-2.875e-12,0.9993
14.0000,-2.416e-11,5.000e-11,-2.875e-12,0.9323
15.0000,-2.583e-11,5.000e-11,-2.875e-12,0.8723
16.0000,-2.754e-11,5.000e-11,-2.875e-12,0.8183

```


Dram_mos.txt Input Data Set to the matlab



DRAM MOS Average Power Plot

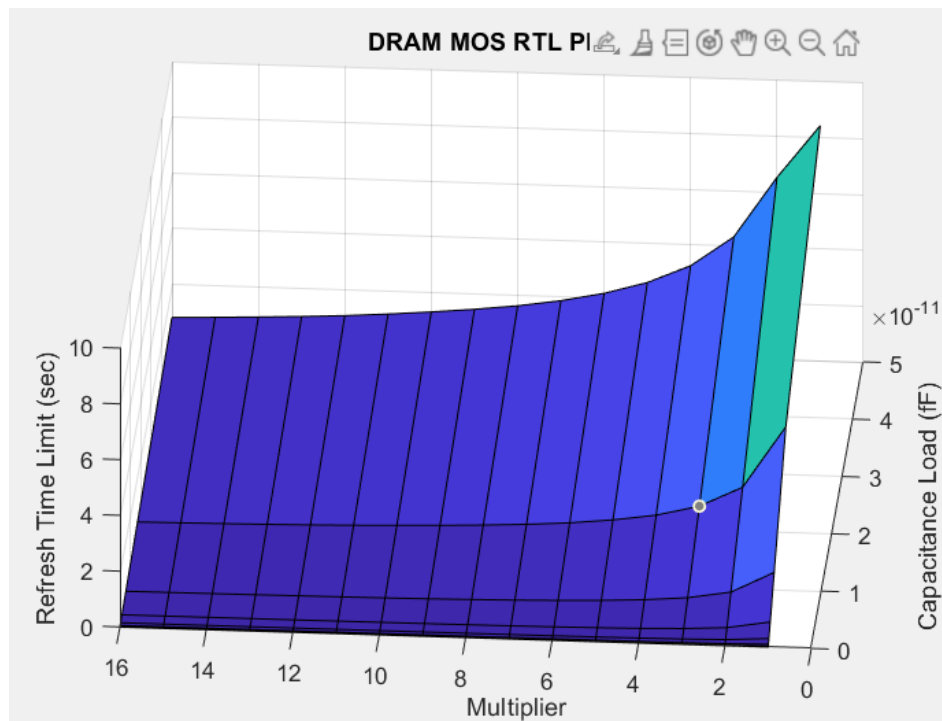

DRAM MOS Average Power Plot

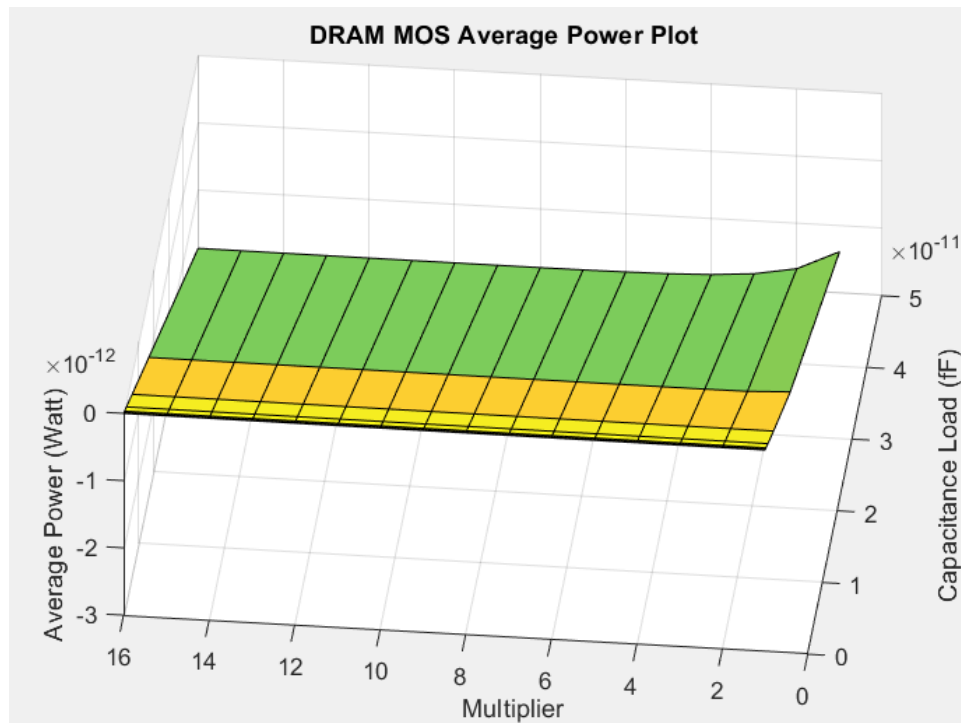

DRAM MOS Average Power Plot

CONCLUSION

Hence the Hspice file was generated for the DRAM using Fin Fet and MOS, after running the HSPICE file, we received a mt0 file and we used a python to extract the mt0 file and generate relevant data, we pass that data into MATLAB and then plot the required 3D graphs, for the statistics regarding the min, max, mean and standard deviation, I am using the python code to extract all the required values.